Report on

THE ENIAC

(Electronic Numerical Integrator and Computer)

Developed under the supervision of the Ordnance Department, United States Army

OPERATING MANUAL

UNIVERSITY OF PENNSYLVANIA

Moore School of Electrical Engineering

PHILADELPHIA, PENNSYLVANIA

June 1, 1946







A REPORT ON THE ENIAC

(Electronic Numerical Integrator and Computer)

Report of Work under Contract No. W-670-ORD-4926

Between

Ordnance Department, United States Army Washington, D. C.

and

The University of Pennsylvania
Moore School of Electrical Engineering
Philadelphia, Pa.

This is copy No. 19 of 25 bound copies of this report.

100 AT THE RESERVE AND ADDRESS OF THE RESERVE AN

 $(2^{n}(4+1)^{n}+\gamma^{n}) = -2^{n}(1+1)^{n} = -2^{n}(1+1)^{n}$

.

0.

7889 E55 1946 V.I.C./ SCOMB

ENIAC OPERATING MANUAL

by

Dr. Arthur W. Burks

and

Dr. Harry D. Huskey

INTRODUCTION TO REPORT ON THE

ELECTRONIC NUMERICAL INTEGRATOR AND COMPUTOR (ENIAC)

O. INTRODUCTION

The Report on the ENIAC consists of five separately bound parts, as follows:

- 1) ENIAC Operating Manual
- 2) ENIAC Maintenance Manual
- Part I, Technical Description of the ENIAC
 Volume I Chapters I to VI
- 4) Part I, Technical Description of the ENIAC

 Volume II Chapters VII to XI
- 5) Part II, Technical Description of the ENIAC
 Included with the Operating Manual and Parts I and II of the Technical Description
 are all drawings (see Table 0.3 below) which are required for understanding these
 reports. The Maintenance Manual assumes access to the complete file of ENIAC
 drawings.

Part I of the <u>Technical Description</u> is intended for those who wish to have a general understanding of how the ENIAC works, without concerning themselves with the details of the circuits; it assumes no knowledge of electronics. •r circuit theory. Part II is intended for those who require a detailed understanding of the circuits. Its organization, to a great extent, duplicates that of Part I so as to make cross referencing between the two parts easy.

The ENIAC Operating Manual contains a complete set of instructions for operating the ENIAC. It includes very little explanatory material, and hence assumes familiarity with Part I of the Technical Description of the ENIAC. The ENIAC Maintenance Manual includes description of the various test units and procedures for testing, as well as a list of common and probable sources of trouble. It assumes a complete understanding of the circuits of the ENIAC, i.e., a knowledge of both Parts I and II of the Technical Description of the ENIAC.

the property of the second

A second second second section (Section 1997) and the second second section (Section 1997) and the section (Section 1997) are section (Section 1997) and the section (Section 1997) and th

1-2-1-1-1-2

-1 - 1 1 1 - 1 - 2 3 8 3 8 1 1 ± 2

1-1-20 x - 1-20 - 10 - 10 - 10

A CONTRACTOR OF THE PARTY OF TH

gette at the territory and the

WELLOW THE STREET

The Report on the ENIAC and the complete file of ENIAC drawings constitute a complete description and set of instructions for operation and maintenance of the machine. The drawings carry a number of the form PX-n-m.

The following tables give the classification according to this numbering system.

TABLE O.1			
Values of n	Division		
1	General		
2	Test Equipment		
3	Racks and Panels		
4	Trays, Cables, Adaptors, and Load Boxes		
5	Accumulators		
6	High Speed Multiplier		
7	Function Table		
8	Master Programmer		
9	Cycling Unit and Initiating Unit		
10	Divider and Square Rooter		
11	Constant Transmitter		
12	Printer		
13	Power Supplies		

	TABLE 0.2
Values of m	Subject
101-200	Wiring Diagrams
201300	Mechanical Drawings
301-400	Report Drawings
1±01-500	Illustration Problem Set-Ups.

The reader of this report will be primarily interested in the types of drawings listed in the following paragraphs. A table on page 4 gives the corresponding drawing number for each unit of the ENIAC.


- 1) Front Panel Drawings. These drawings show in some detail the switches, sockets, etc., for each panel of each unit. They contain the essential instructions for setting up a problem on the ENIAC.
- 2) Front View Drawings. There is one of these drawings for each kind of panel used in the various units of the ENIAC. These show the relative position of the trays and the location of the various neon lights. Since these drawings show the neon lights, they can be used to check the proper operation of the various units.
- 3) Block Diagrams. These drawings illustrate the logical essentials of the internal circuits of each unit. That is, resistors, condensers, and some other electrical details are not shown; but complete channels (paths of pulses or gates representing numbers or program signals) are shown in all their multiplicity. These drawings will be of interest to those who are interested in Parts I and II of the Technical Report.
- 4) Cross-section Diagrams. These drawings are electronically complete except that only one channel is shown where there is more than one. Thus, these drawings show every resistor and condenser and any other electronic elements: belonging to any circuit. These drawings will be of particular interest to the maintenance personnel and to those reading Part II of the technical report.
- 5) Detail Drawings. All other drawings of the ENIAC come under this heading. A complete file of drawings is available at the location of the ENIAC.

Table 0.3 ENIAC DRAWINGS

Unit	Front Panel	Front View	Block Diagram	Cross - Section
Initiating Unit	PX-9-3 02 9-302R	PX-9-305	PX-9-307	
Cycling Unit	PX-9-303 9-303R	PX-9-304	PX-9-307	
Accumulator	PX-5-301	PX-5-305	PX-5-304	PX-5-115
Multiplier	PX-6-302 6-302R 6-303 6-303R 6-304 6-304R	PX-6-309	PX-6-308	PX-6-112A 6-112B
Function Table	PX-7-302 7-302R 7-303 7-303R	PX-7-305	PX-7-304	PX-7-117 7-118
Divider and Square Rooter	PX-10-301	PX-10-302	PX-10-304	
Constant Trans- mitter	PX-11-302 11-302R 11-303 11-303R 11-304 11-304R	PX-11-306	PX-11-307	PX-11-116 11-309 (C.T. and R.
Printer	PX-12-301 12-301R 12-302 12-302R 12-303 12-303R	PX-12-306	PX-12-307	PX-12-115
Master Pro- grammer	PX-8-301 8-301R 8-302 8-302R	PX-8-303	PX-8-304	PX-8-102

Other drawings of particular interest:

Floor Plan	PX-1-302	IBM Punch and	PX-12-112
A.C. Wiring	PX-1-303	Plugboard	PX-12-305
IBM Reader and	PX-11-119	Pulse amplifier an	
plugboard	PX-11-305	Block Diagram	PX-4-301
Intercon	nection of Multipl	lier and Accumulators	PX-6-311
		r and Accumulators	PX-10-307

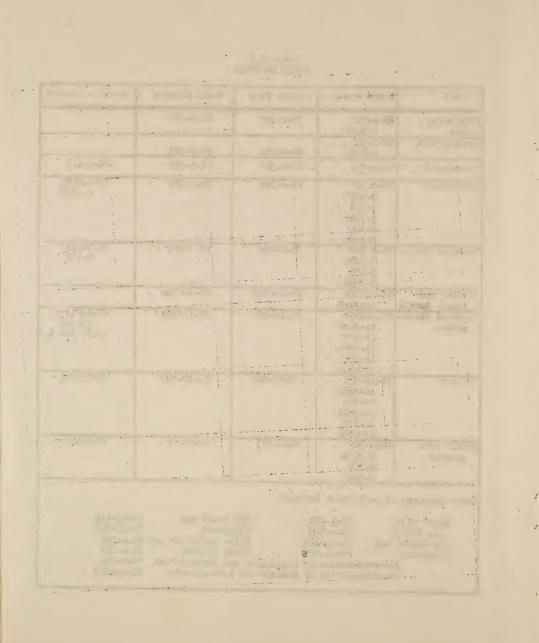

The front view drawings and the large front panel drawings (whose numbers do not end with "R") are bound as a part of the Operator's Manual.

Included with the report is a folder containing all the drawings listed in the above table except the large front panel (see above) drawings.

1. GENERAL INSTRUCTIONS FOR OPERATING PERSONNEL

- 1. Inform maintenance personnel immediately of any trouble and note same in the log book.
- 2. Occasionally check the filament fuse indicator lights (refer to front view drawings bound in this volume); if any are cut turn off the d-c power (switch is located on a-c distribution panel, see PX-1-304).
- 3. If ENIAC shuts down from overheating do not try to restart; call maintenance personnel. If any panel runs consistently much hotter than the others, do the same.
- 4. The d-c power should be turned on only with operation switch (either on cycling unit or on the hand control) turned to "continuous". After the d-c has been on a few seconds it may be turned to either of the other two positions. Failure to follow this rule causes certain d-c fuses to blow, -240 and -415 in particular.
- 5. As a general matter certain units not being used may have their heaters turned off. In such cases it is unnecessary to remove the d-c power or even to turn off the d-c power when turning on these units. On the other hand the three panels of the constant transmitter must be turned on or off simultaneously.
 - 6. Do not remove any covers, front or back.
- 7. Do not open d-c fuse cabinet with the d-c power turned on. This not only exposes a person to voltage differences of around 1500 volts but the

and the second of the second o 70 f 1 (20 10 TE)

person may be burned by flying pieces of molten fuse wire in case a fuse should blow.

- 8. Padlocks are provided for locking the d-c power off. Lock the power off and carry the key with you as long as you are working on the machine.
- 9. Do not remove accumulator interconnector plugs, or function table or IEM machine connector cables, while the d-c is on. All other front panel plugs may be safely moved while the power is on.
- 10. Do not pull directly on wire or cable; always use the plug case as a grip.
 - 11. Do not put sharp bends in cables or hang anything on them.
 - 12. Do not leave cables dangling on the floor.
- 13. Do not pound or force plugs; if they do not respond to steady pressure notify maintenance personnel.
- 14. Do not leave IBM cable connectors or portable function table connectors lying out in the open, keep in the receptacles provided. Also, make use of the ramps to protect the cables of any such units which are connected to the ENIAC.
 - 15. Do not force any switches.
- 16. Keep the door to the room closed to keep out dust, avoid stirring up or producing dust.
- 17. Always move the portable function tables with care. Keep the brakes on when not moving them.

2. PROBLEM SET UP REMARKS

2.1. NEED FOR SYSTEMATIC CHECKS

Since the ENIAC makes use of a hierarchy of channels (first, in that a

· The section of the section of the section of number of units may be carrying on computations simultaneously; second, in that it always handles ten to twenty digits of a number simultaneously; and third, in that certain units use a coded system giving four channels for each digit) running a standard check problem is not a sufficient check on the accuracy of the results. Thus, in arranging a problem for the ENIAC provision should be made for occasional systematic checks of all the units.

Procedures for systematic checking are described in some detail in the maintenance manual. Brief procedures will be outlined here for the numerical units. The following test procedures are not comprehensive tests and the experienced operator will perhaps use variations of them. In particular, the tests given below are not designed to check the operation of the various program controls. However, they are designed to check the numerical circuits in each unit and to a considerable extent check the program control used to carry out the test.

2.2. TESTING AN ACCUMULATOR

Cards should be prepared as follows:

- 1. P 11111 11111
- 2. P 00000 00001

The numbers should be so placed on a card that one group in the constant transmitter, say $A_{\rm IR}$, corresponds to these numbers. Next, a master programmer stepper should be used to transmit the first number into the accumulators which are to be tested eighteen times. At this time the accumulators should read

M 99999 99998

and all stages of each decade have been checked as well as the delayed carry-over circuits. Now the stepper (used above) should cause the reader to read the next card and the number to be transmitted to the accumulators twice. This should

Contractor 1

Acres de la companya del companya de la companya del companya de la companya de l

Miles Inches

give

P 00000 00000

and checks the direct carry-over circuits. Note that this test assumes that the significant figure switch is set to "10". If this is not so the operator can modify the above procedure to take care of this.

This test does not check the following circuits (for a complete checking procedure see the maintenance manual):

Transmission circuits
Clearing circuits
Repeater ring

Input channels (except for the one used)
Program controls (except for the one used)

2.3. TESTING THE MULTIPLIER

The following set of cards should be prepared.

Card		Multip A _{LR} ((say)
1	P	00000	00000	P	11111	11111
2	P	11111	11111	P	11111	11111
3	P	11111	11111	P	22222	22222
			* * * * * * * * * * * * * * * * * * * *	• • • • • • •		
10	·P	11111	11111	P	99999	99999
11	P	22222	22222	P	11111	11111
12	P	22222	22222	P	22222	22222
• • • • • • • • • • • •				• • • • • •		
82	P	99999	99999	Р	99999	99999
83	IP	11111	11111	M	11111	11111
84	М	11111	11111	P	11111	11111
85	М	11111	11111	M	11111	11111

CONTRACTOR OF THE PARTY OF THE

AND MADE OF

On a second set of cards, or on these same cards in different fields the proper answers should be punched. Note that these answers will depend upon when ten or twenty digit products are used, that is, whether the product accumulators are used as ten or twenty digit accumulators.

There are two methods of using these cards to check the numerical circuits of the multiplier. One is to have the answer on the same card and arrange for its transmission to the product accumulators with its sign changed (or the sign of one of the factors may be changed). In this case the whole sequence of cards in run and the presence of "zero" in the product accumulators indicates (with high probability since there could be compensating errors) that the numerical circuits are all right.

A second method is to run the test and cause the answers to be punched on other cards. These results may then be compared with standard answers by use of the reproducing punch.

This procedure does not check the following:

Rounding off circuits

Program controls (other than the one used).

2.4. TO TEST A FUNCTION TABLE

An accumulator is used to build up the argument. A program control on the function table has its function switch set to "-2" and a second switch has its argument set to "+2".

The programming is so arranged that the "-2" program is activated and the output sent to an accumulator associated with the printer. The result is punched on a card, "one" is added to the argument, and the process repeated.

LOCATION STORY AND

The master programmer can be used to repeat the "-2" program 96 times and then alternately activate the "-2" and the "+2" program four more times. (Or various other schemes may be devised to obtain all 104 entries to the function table.) The cards punched in this manner can then be compared with a standard deck.

Note that the above check is <u>not</u> a systematic check of the numerical circuits as a whole. In other words this check should be repeated if any switches on the portable table (or on panel No. 2) are changed.

Furthermore, the above procedure does not check the various program controls of the function table.

2.5. TO TEST THE DIVIDER AND SQUARE ROOTER

The divider and square rooter can best be checked by performing test division problems and square root problems. Drawing PX-10-111 gives the meons which should be lit at various places in the process. The operator can check against this by going through the problem at one addition time.

2.6. CONSTANT TRANSMITTER TEST PROCEDURE

The 1, 2, 2', 4 channels in the constant transmitter can all be checked simultaneously by reading cards with nine punches on them. Since it is undesirable that the same number be punched in all columns of a card (this weakens a card increasing the probability of "jamming" in the feeding mechanism of the IBM machines) it is suggested that cards be prepared as follows.

- 1) 9's in groups $A_{\rm LR}$ and $B_{\rm LR}$
- 2) 9's in groups C_{LR} and D_{LR}
- 3) 9's in groups E_{LR} and F_{LR}

No. of the second secon

- 4) 9's in groups G and H IR
- 5) Four more cards similar to above but with minus punches.

The programming should be arranged so that the numbers are transmitted into accumulators when they can be inspected visually or perhaps punched on other cards and compared with a standard deck using the reproducing punch.

Note that $J_{\rm LR}$ and $K_{\rm LR}$ should be checked in a similar manner. (These only need be checked for the numbers used in the set-up provided they are rechecked any time that some of the switch settings are changed.)

This procedure does not check all the program controls.

2.7. PRINTER TEST PROCEDURE

The printer can be tested by causing all possible digits in each channel to be punched and by checking the PM delays. The following cards should be prepared.

- 1) P 01234 56789
- 2) P 11111 11101
- 3) P 11111 11011

.

- 10) P 01111 11111
- 11) P 11111 11111

The programming should be arranged to cause the numbers on the test cards to be read by the IBM reader, transmitted to the printing accumulators, and the result punched. The resulting cards may be compared with a standard deck by use of the reproducing punch.

Card number one has the numbers 0 to 9 punched in it to prevent the same digit from being punched all across a card.

and the second second

MARKET WILLIAM TO THE

0.50 to 1.

2002 1101 1 7

4

0.00 0.00 0.00

ACCUSED TO A SECOND

If any decades of the master programmer are used in printing they may be checked at this time by transmitting the program pulse (used to activate the above sequence) into each decade direct input.

This constitutes a complete test of the printer.

2.8. TESTING FOR TRANSIENT FAILURES

If transient failures are suspected a master programmer stepper should be used to repeat the appropriate test (such as one of those above) a large number of times.

In case of an <u>accumulator</u> this can be done using only one card (say, P 99999 99999) and using a second program control set to αC (receive on α and correct) to obtain the one pulse in the units decade.

For the <u>multiplier</u> it becomes necessary to punch the answers on the cards with the factors (see 2.3) and cause these to be transmitted to the product accumulators for each multiplication. If more than ten digit answers are used the adjusted answer to card 83 must be carefully prepared in order to get minus the answer from the constant transmitter to the product accumulators (since the constant transmitter only complements at most ten digits at a time).

Repetition of a <u>function table</u> test is straight forward. It may be worth while to receive into a twenty digit accumulator and repeat the transmission 10^4 times, say, and see if the proper number is obtained.

The square root of zero is perhaps the easiest test to repeat on the divider-square rooter.

The <u>constant transmitter</u> can be caused to transmit any group repeatedly to some accumulator. Dust particles may cause transient relay failures, so avoid stirring up dust in the ENIAC room. Also, if any relay case is removed, always


The stand of the standard of t

And the second s


All in the first of the first o

replace in exactly the same position in order not to disturb dust inside the case.

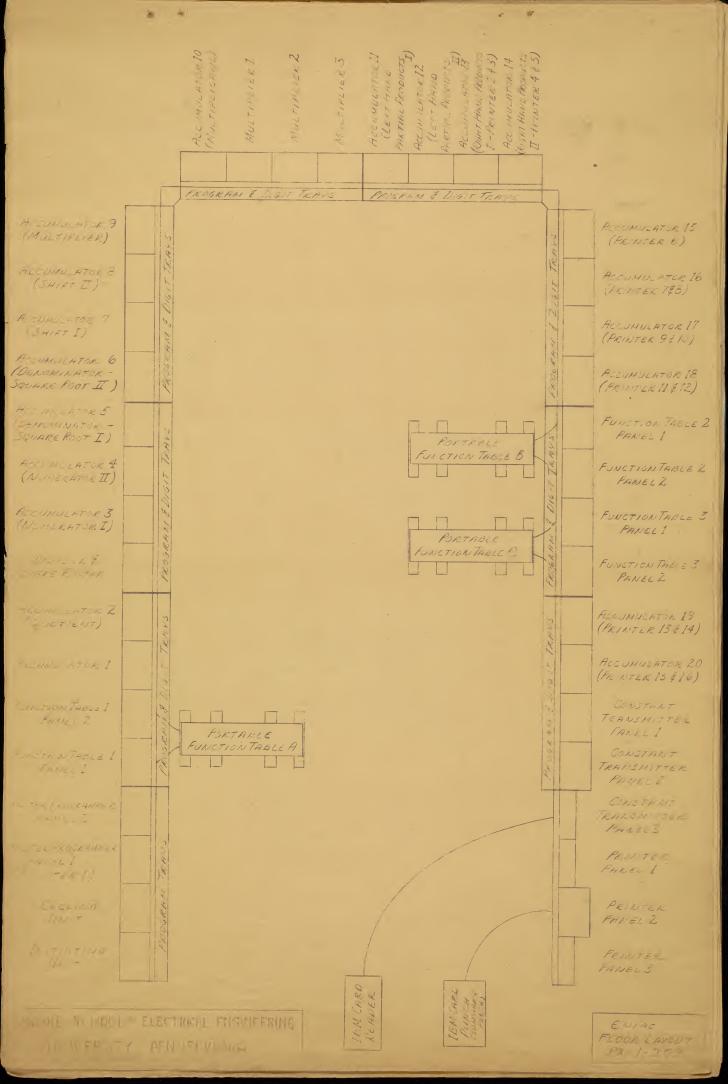Transient failures in the <u>printer</u> are probably relay failures. See maintenance manual for list of probable failures.






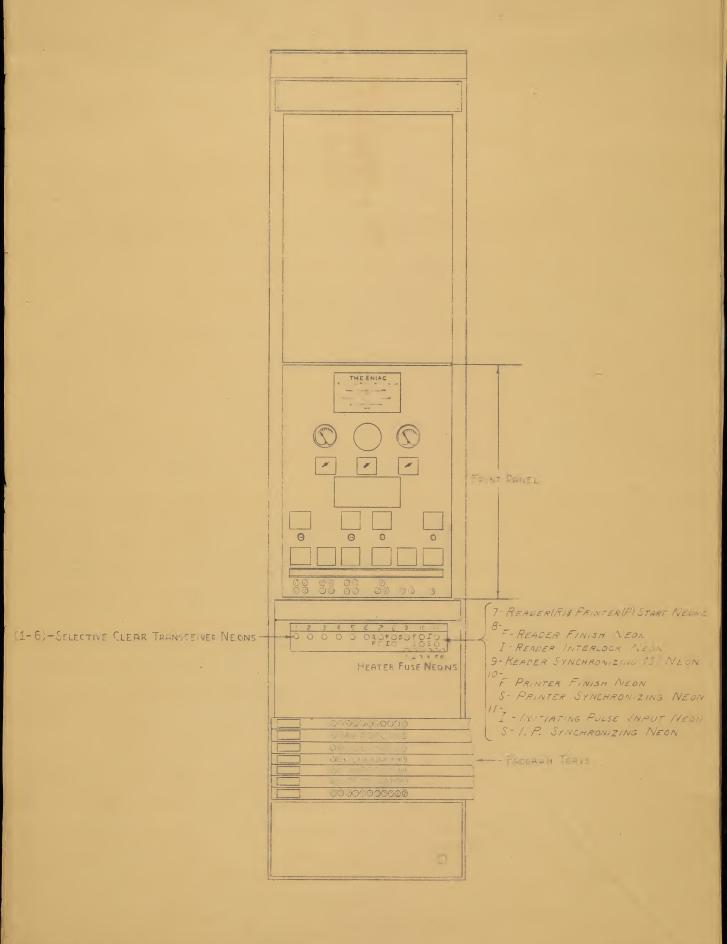

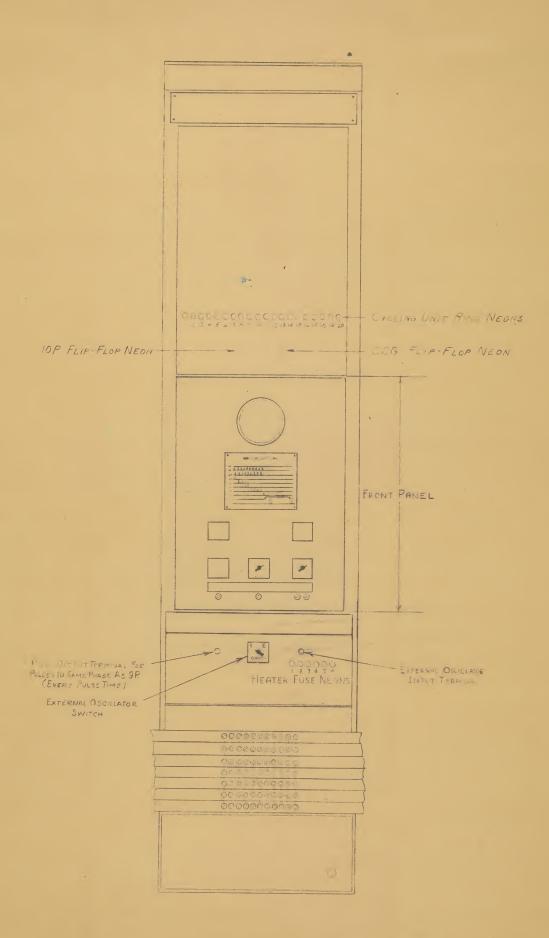MEDIE SCHIOL OF ELECTRISING IN MESSAGE AN OBJUSTY OF PERMITTION OF FASSIT ASTA







0 90 0 10 0 10 0 9 40 9 30 9 20 DECADE NUMBERS 0000000000 "STADE FRANCE CONTENTS -- FRONT PANE * * * * * * * * (1-1/8; No ! -- 1. 15-12 Test -- 48-41) HEATER PLUE WEATS 50607 303010011012 REPEATER VEDIS 123456

MODRE LEADLER SLECTIFF ENSINEERING VANCLER OF SLECTIFF ENDINE

0


ABENIALLATOR FEOLT PIEW PI-5-208



PESET FLIP-FLOP NEIN PROBLEM RIVE NEONS 2 1 1 1 1 1 1 TIPNSCE LER N_ONS (1-24) HEATER FUSE NEONS HEATER FUSE NEONS

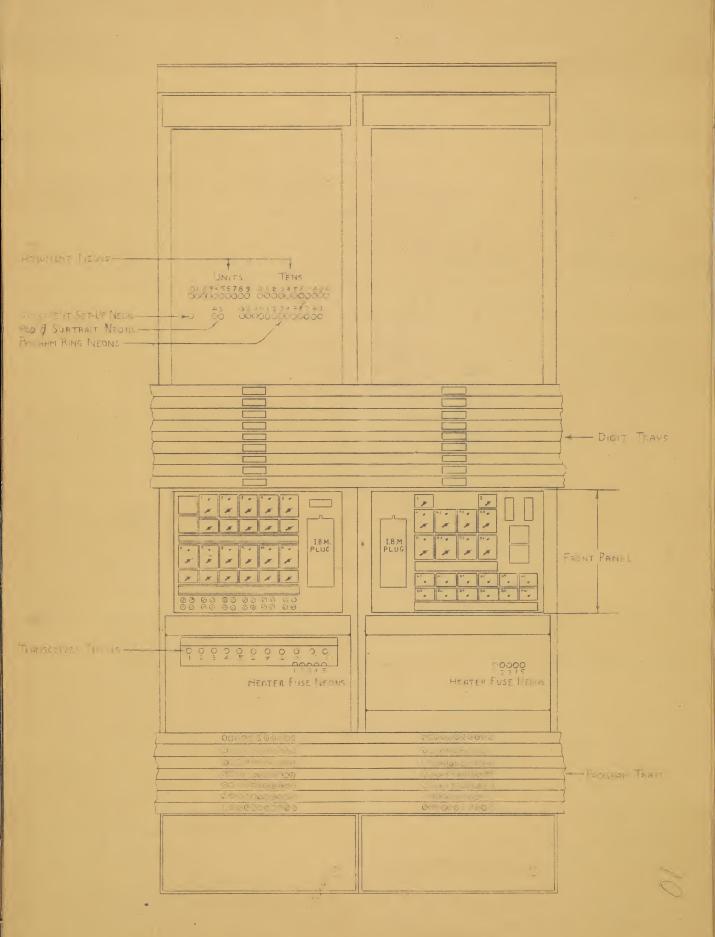
MESTE SCHOOL & SLEEK KILDE SWEDNIETING UNIVERSITY & LEVY YEARS & His N Demonstrated in Plays 1 miles 04 - 6 - 609






MODEE STHOOL OF ELECTRICAL ENGINEERING

FUNCTION. TABLE FINCTION PI-2-305

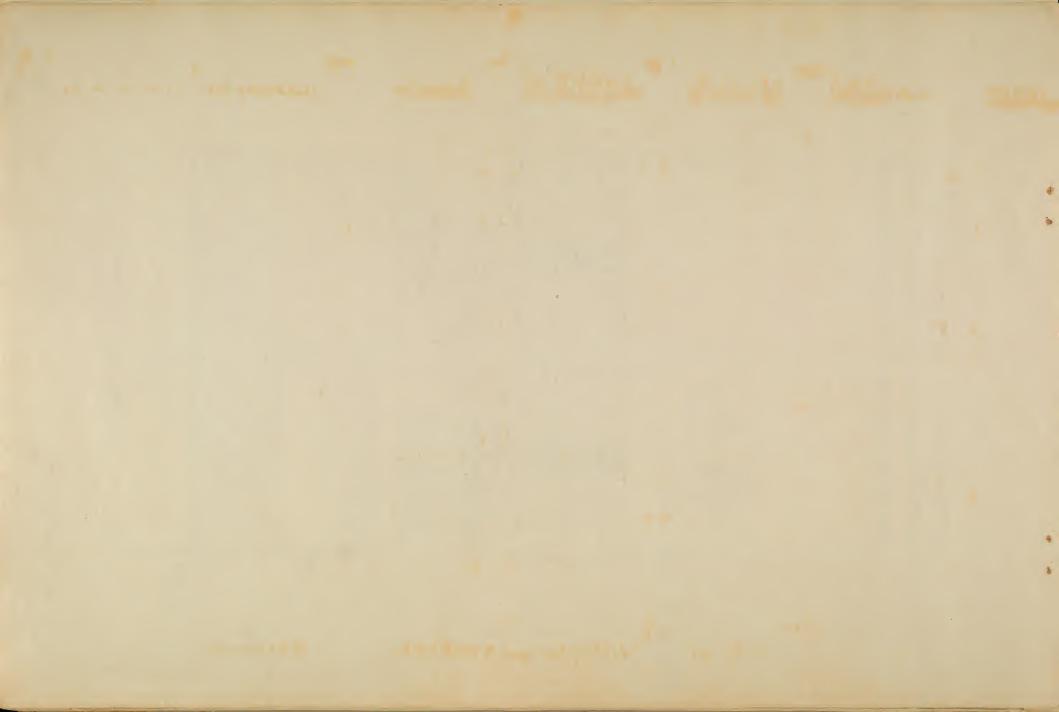

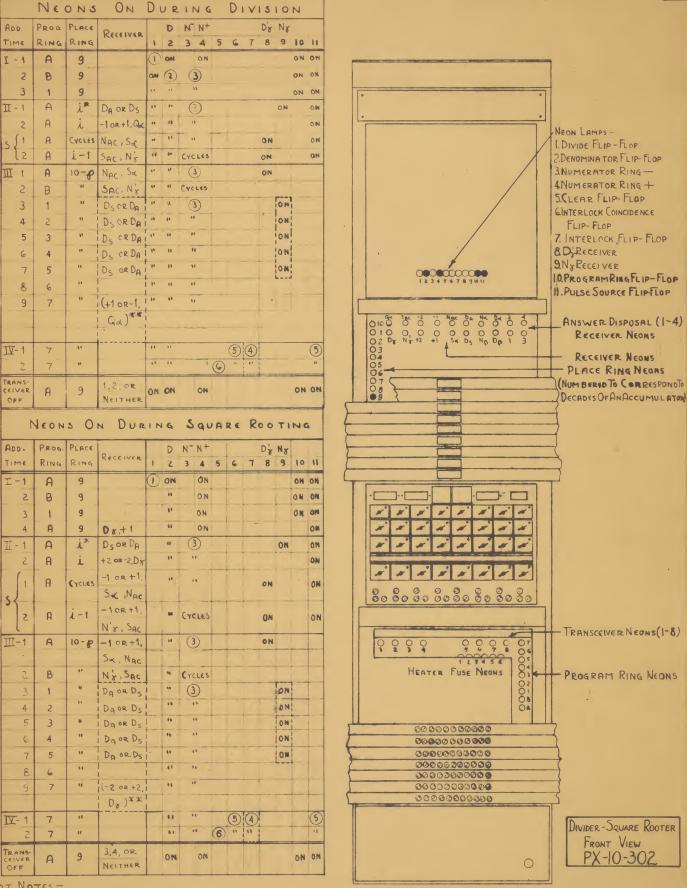

FOOT NOTES -

ON IF PREVIOUS PROGRAM WAS A DIVISION

2) ON IF DENOMINATOR IS POSITIVE WHEN RECEIVED IN DENOMINATOR ACCUMULATOR

3) IF, BEFORE DENOMINATOR ISADDED TO OR SUBTRACTED FROM NUMERATOR, THE NUMERATOR IS POSITIVE, NEON *4 IS ON; OTHERWISE NEON # 3 IS ON.


4) GOES ON WHEN INTERLOCK PULSE IS RECEIVED.

5. GO ON ONE ADDITION TIME AFTER III-9

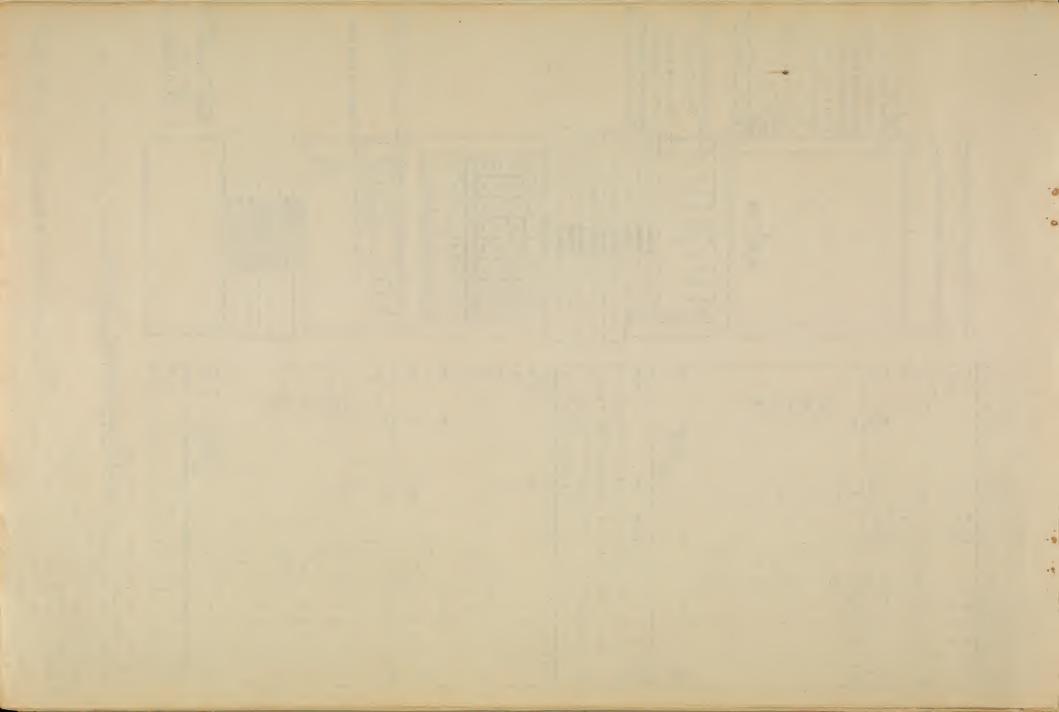6. GOES ON: a- IN NI CASE, TWO ADDITION TIMES AFTER III-9. b-IN I CASE, IN WHICHEVER OCCURS LATER: TWO ADDITION TIMES AFTER III-9 OR ONE ADDITION TIME AFTER NEON ?

** ONLY IF NO OVERDRAFT RESULTS.

9 ≥ i ≥ 10-p WHERE P IS THE SETTING OF THE PLACES SWITCH




Textererore The text of the te 7 2 9 4 4 Y 9 9 4 4 7 X 7 7 7 7 7 7 X X X * THEMSCEIVER ! HEATER FUSE NEONS HEATER FUSE NECHS

MILKE JUNION - I STALL SELECTIONS AND F

HARRY WITH



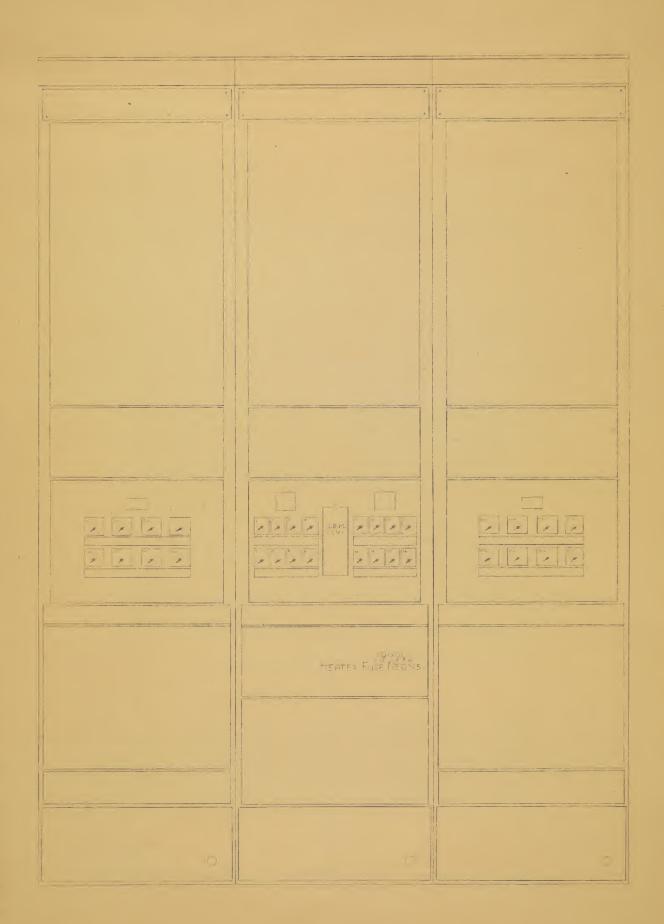

NOORE SCHOOL OF ELECTRICAL ENGINEERING


PRINTER (FULL DOL) ENGLISE





-DECAGE NEONS -STEPPER NEONS FRONT PANEL ୍ଟିଲ୍କ ପ୍ରକ୍ର ଅନ୍ତ ହୌରୁପ୍ର ହିନ୍ଦ୍ର - STEPPER INPUT WEGINS 123456 HEATER FUSE NEONS HEATER FUSE NEONS


THE WARDLEST ELECTRICAL EVENTS OF THE PARTY OF PERSONS


MISTER MENTEMBER MELTEMBER

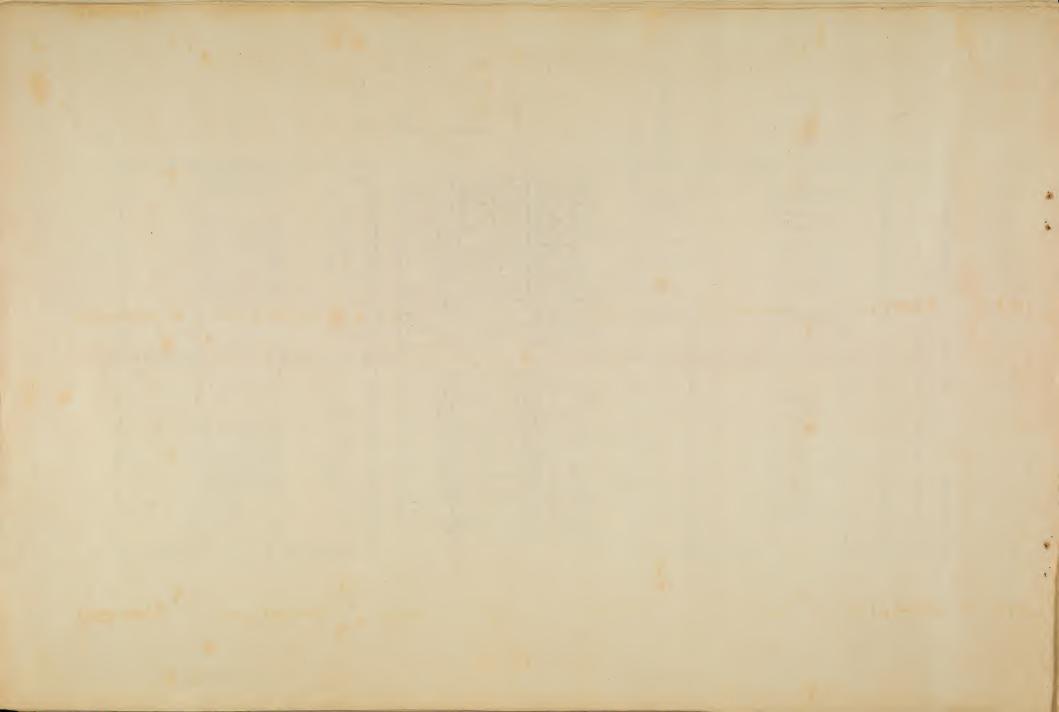


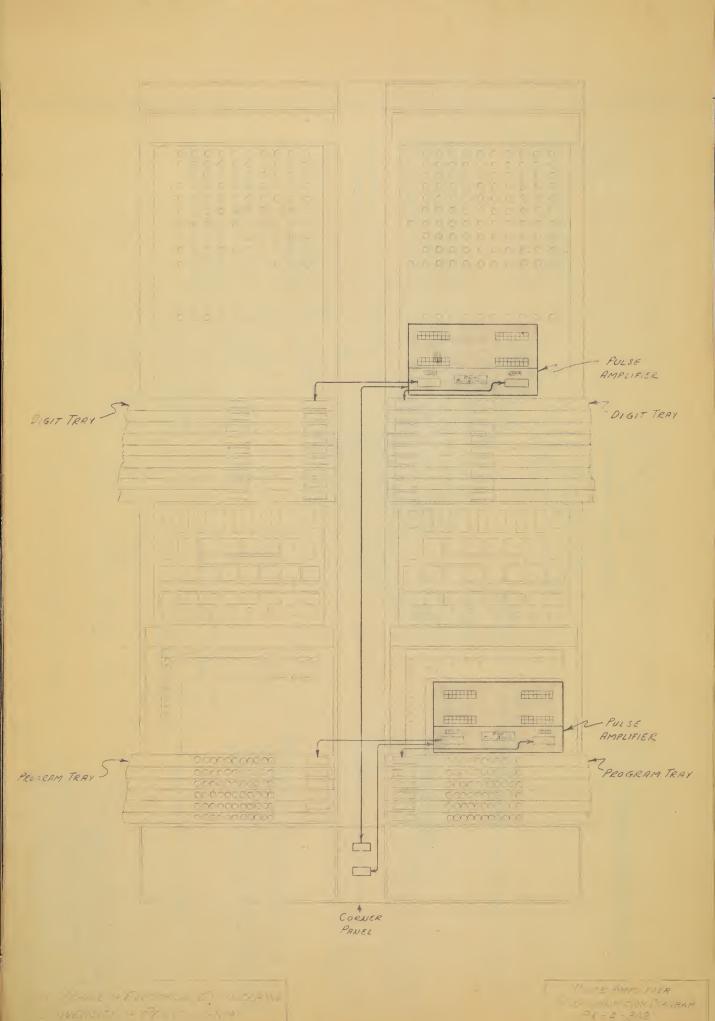


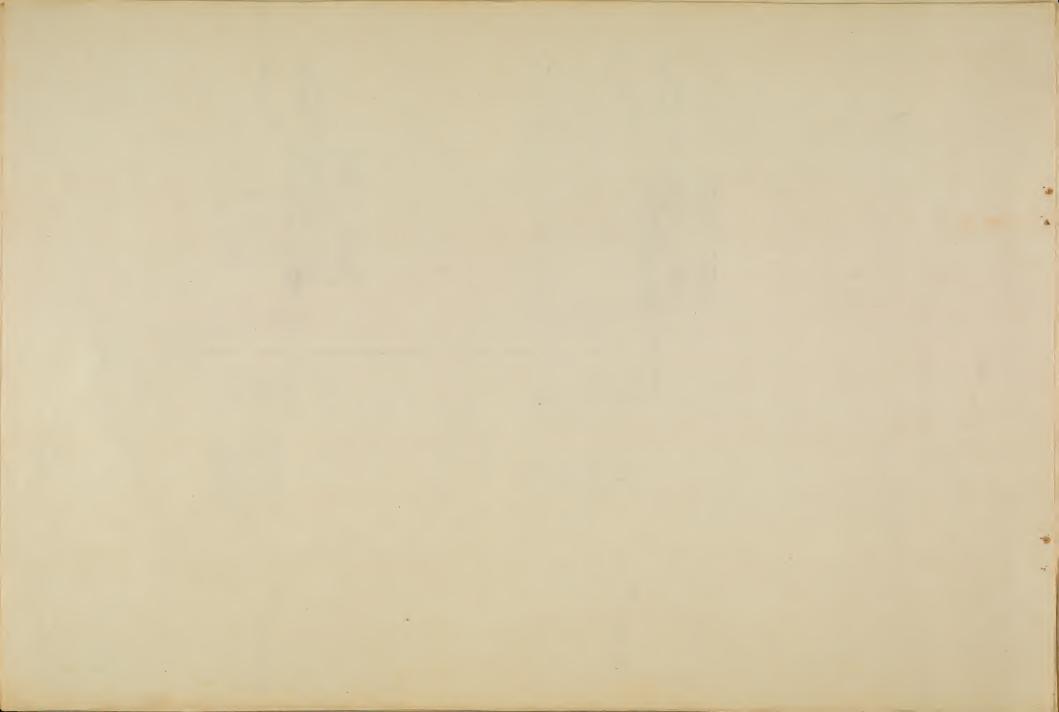

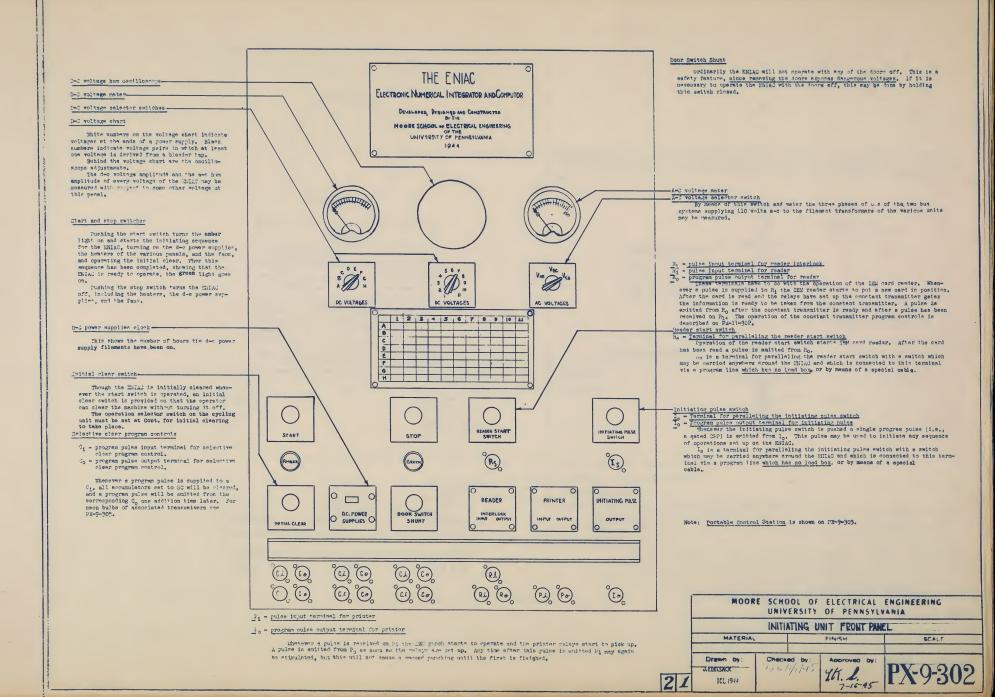

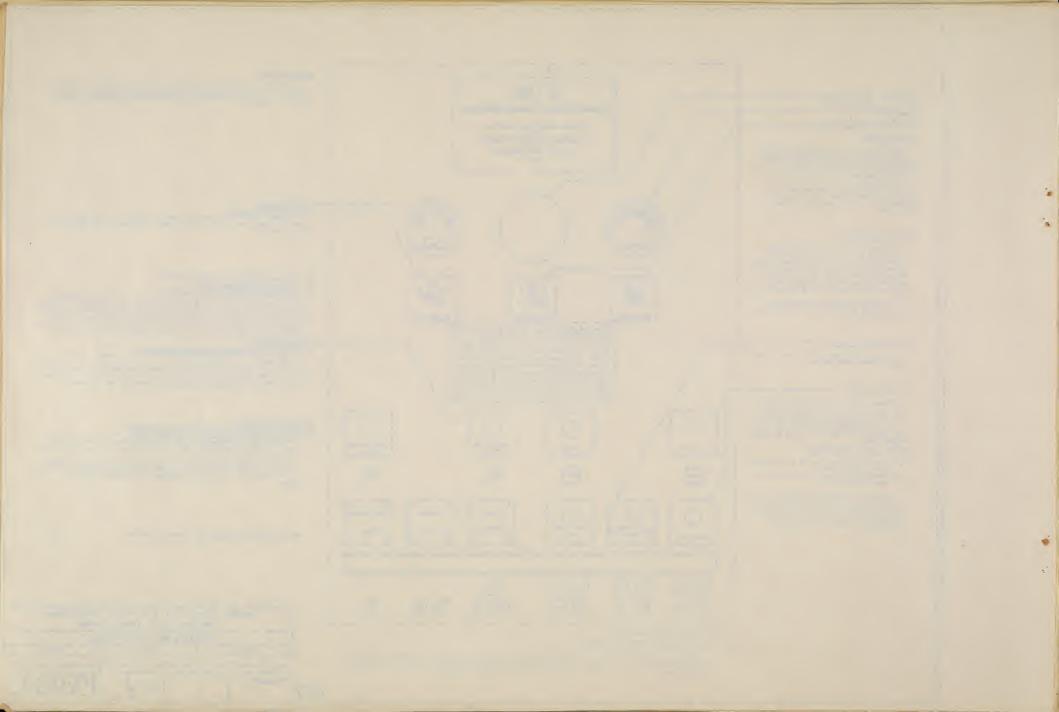

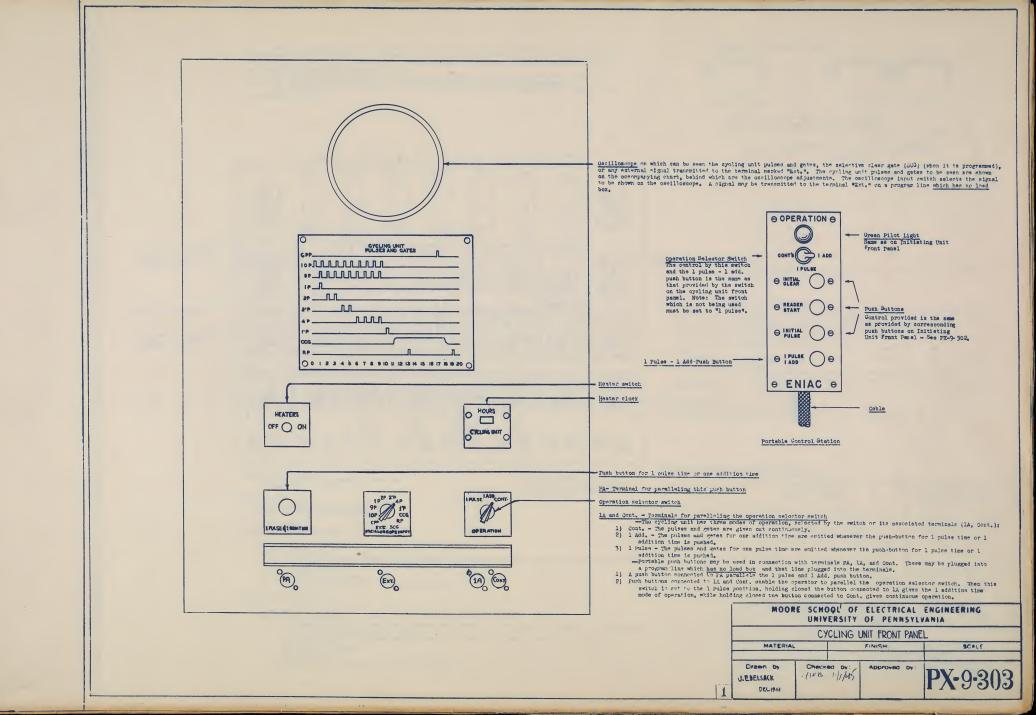


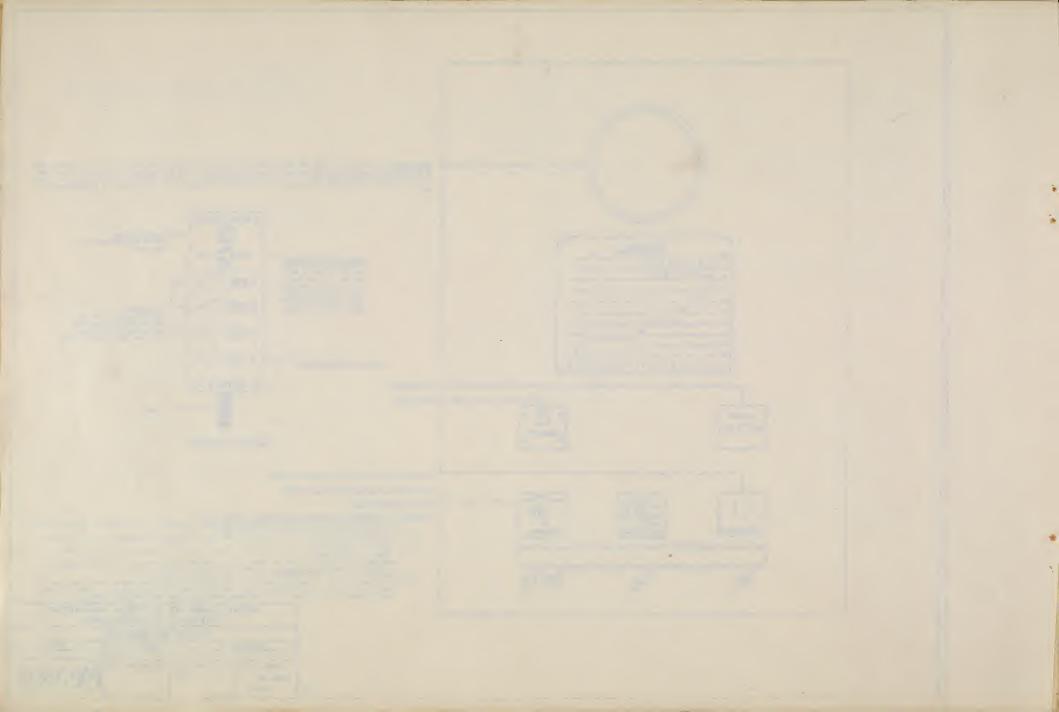

The digit terminals are to be connected to the digit trunks (trays) (see $P_x = 9-90$) by the digit cables for receiving and transmitting numbers. The operation of these terminals is governed by the program controls of the accumulator. (Thus digit pulses transmitted on a trunk to which the Δ terminal is connected are received only if

accumilator, (Thus digit pulses transmitton on a trunk to which the Accuminating connected are received only if the accuminator is programmed to receive on of).

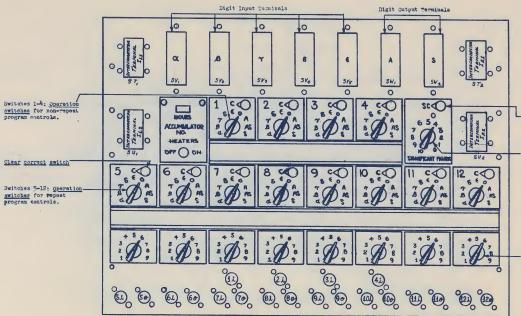Nultiplication by powers of ten may be accomplished by means of shifters (PX-1-104) which transpose the digit wires. Shifters must be placed only in digit input terminals, not in digit output terminals, paleters (PX-1-109) are used in connection with the significant figures switch; they may be placed only in digit output terminals.



Terminals 11, 21,..., hi
Program pulse input terminals for non-repeat program controls 1-4 respectively.

Program pulse input terminals for repeat program controls 5-12 respectively.

Non-repeat program controls 1-4.

These operate for one addition time and emit no program output pulse. Each control consists of

1) Program pulse input terminal (when atimulated with program pulse causes program control to program operation in accordance with its switch settings)

Terminals 50, 60120

Program pulse output terminals for

repeat program controls 5-12 respectively.

2) Operation switch 3) Clear-correct switch

4) Associated receiver (For meon bulbs see PX-5-505)

Repeat program controls 5-12.

These operate for n additions times, where n is the setting of the repeat switch.

Each control consists of

1; Frogram pulse input terminel (when stimulated with program pulse causes program control to program operation in accordance with its switch settings).

2) Program pulse output terminal (emits program pulse at end of nth addition time)


3) Operation switch 4) Clear-correct switch

5) Repeat switch

6) Associated transceiver (For meon bulbs see PX-5-305)

Accumulator Interconnection - Diagram



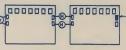

10 decade accumulator

20 decade accumulator

V: Acc. interconnector cable (vertical) (PX-5-121)

H: Acc. interconnector cable (horizontal) (PX-5-110) X indicates position of acc. interconnector terminal load box (PX=5-109)

Note: Each of the 2^{ll} program controls of the 20 decade accumulator governs the operation of all decades and of the common programming circuits of both accumulators.

Selective clear switch

If this switch is set to SC the accumulator is cleared whenever a program pulse is transmitted to one of the selective clear inputs of the initiating unit.

Interioral figures skitch

This switch determines which decade (if any) is cleared to 5 instead of 0 whenever the accumulation is cleared and on which line the subtract pulse is transmitted on a subtract transmission. It does not govern the deletion of non-significant digits; this must be done by means of deleters (PX-L-109) (When the switch is set to m, deleter number nishould be used, stc.)

If the switch is set to m, decade 10-m (counting from the right) is cleared to 5, and the

When a 20 decade accumulator is formed, the two significent figure switches are to be used as

(A) When 9 or less significant figures are desired, the left hand switch is set to the number desired and the right hand switch to 10, (2) When 10 or more significant figures are desired, the left hand switch is set to 10 and the

right hand switch set so that the sum of the two switch readings equals the number of significent figures desired.

Repeat switches for

repeat program controls 5-12

Each awitch governs the number of addition times its repeat program control operates.


Operation switches and clear-correct switches:


Operation switch setting	Operation programmed by operation switch	Operation programmed by clear-correct switch if set to C.
nox e g	Receive on od digit input terminel Receive on # digit input terminel Receive on # digit input terminel Receive on & digit input terminel Receive on & digit input terminel	A correct pulse (an inter- nally gated 1° pulse) is placed in the units decade at <u>each</u> addition time.
A Aus S	Nothing Pressmit on add digit output terminal Transmit on both add and subtract digit output terminal Transmit on subtract digit output terminal	The accumulator is cleared at the end of the last addition time of the program

MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA

ACCUMULATOR FRONT PANEL MATERIAL FINISH

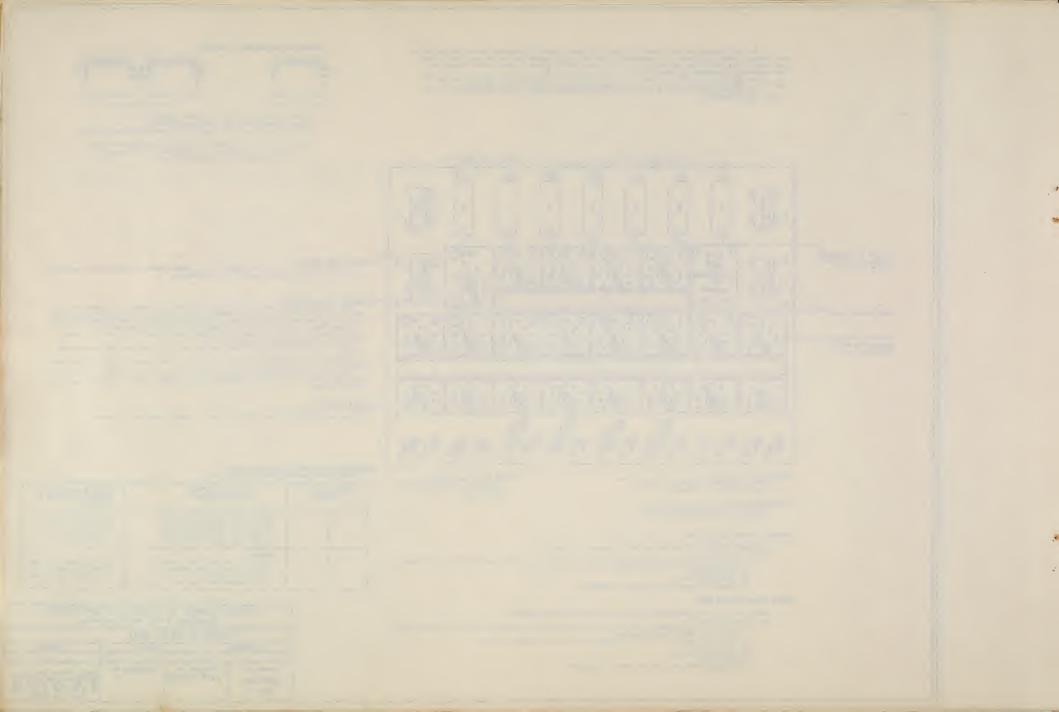SCALE. Approved by: aws 10/12/45 J. EDELSACK DEC. 1944



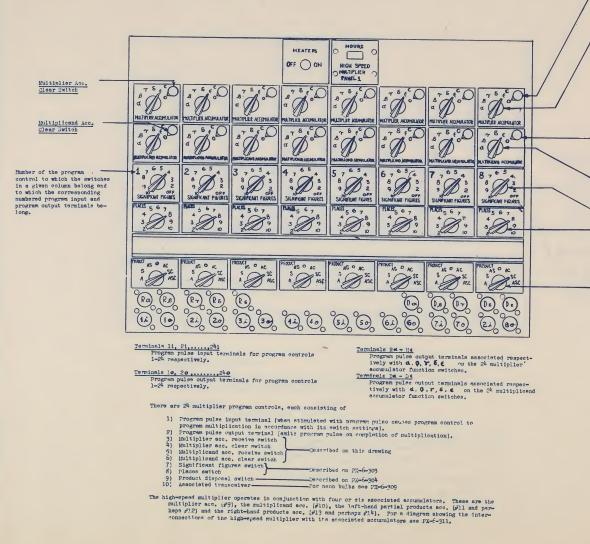

Multiplier Accumulator Clear Switch

This governs the clearing of the multiplier acc, by means of the static cable running into the multiplier acc. By plug-in unit. If this switch is set on C, the multiplier is cleared during the last addition time of the multiplication.

Multiplier Accumulator Receive Switch

Whenever a program pulse is received on a program input terminal of a given program control, a pulse is irredictely emitted from NN= \mathbb{H}_{δ} , or not at all, accordingly as the multiplier accidentions switch of that program control is set one \mathcal{A}^{β} , or to respectively. These pulses may be used to cause the multiplier acc. to receive the multiplier during the next addition time by having them termsmitted to properly act multiplier acc, program controls, i.e. by connecting acting to five program pulse inputs of the multiplier acc. [#9] and setting the corresponding operation switches to receive on \mathcal{C}^{β} craspectively.

It is to be noted that all 24 multiplier program controls cause pulses to be emitted on Rg -Re so that only five multiplier acc, program controls are required to receive all 24 multipliers.

Eultiplicand Accumulator Clear Switch

This operates the same as the multiplier acc, clear switch except that it governs the clearing of the multiplicand acc.

Multiplicand Accumulator Receive Switch

This functions the same as the multiplier acc, receive switch except that it gives out program polynes on terminals DoC to Dg and may be used with the multiplicand acc, (#10).

Significant Figure Switch


Multiplier Flaces Switch


Product Disposal Switch

MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA

HIGH-SPEED MULTIPLIER FRONT PANEL NO.1

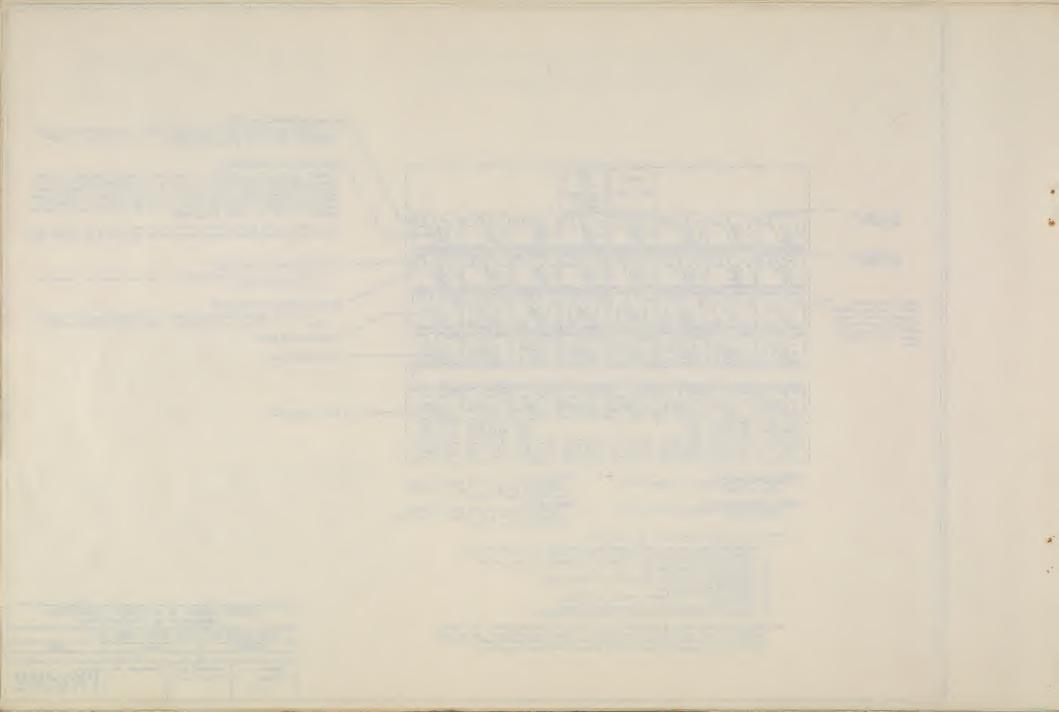Drawn by: Cherked by: Approved by: LEDELSAKK DEC. 1944



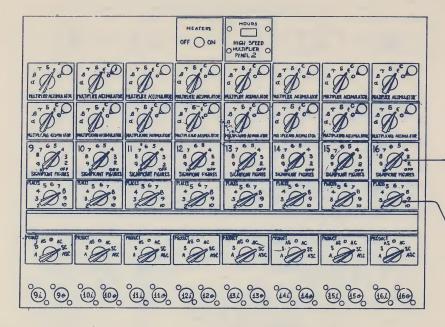

Time schedule for multiplication

A multiplication requires from 6 to 14 addition times (depending upon the setting of the places switch) including the time required for receiving the multiplier and multiplierand, but not including the time required for disposal of the product.

Addition time Operation (Program input pulse received at end of 0th addition time)

1	Multiplier and multiplicand received	
2	Five round-off pulses transmitted to left-hand product acc. (#11, 12)	
3	Multiplicand multiplied by first place (10th decade) of multiplier	
	and left and right hand components transmitted to left and right hand	
	product acc.	
p+2	This is continued up to the p+2d addition time, where p setting of	
-	pleces switch	
p+3	Complement corrections are made when necessary.	
p+4	Accumulated left hand products are added into accumulated right hand	
•	products.	
(Program output pulse and	enswer disposal pulsesemitted at end of p+4th eddition time)	
p+3 p+4	Complement corrections are made when necessary. Accumulated left hand products are added into accumulated right hand products.	

Significant Figures Switch

This switch may be used to give a varieble round-off; i.e., a product which is rounded off in a different place for each program control. This switch governs the addition of 5 pulses into the proper place of the left-hand product acc. (#II, 12) during the second addition time of the multiplication.


It does not control the deletion of the non-significant digits of the product nor the plecing of the subtract pulse in the proper channel of the product on a subtract transmission. Since these vary with the setting of the significant figures switch, they must be taken care of at the accumulator which receives the product. Hence in cases where every product is to be rounded-off to the same number of places, it is best to use the round-off fecilities of the right-hand product acc. [#13, 14].

Places Switch

This governs the number of places of the multiplier that are to be used in the multiplication. The multiplier digits are used from left to right, so that the most significant digits are used first. The places referred to are the places of the multiplier acc, counted from the left.

The places switch is completely independent of the significant figures switch. The reason for this is that all digits of the multiplicand are used in the multiplication process. The only purpose of the places switch is to save time.

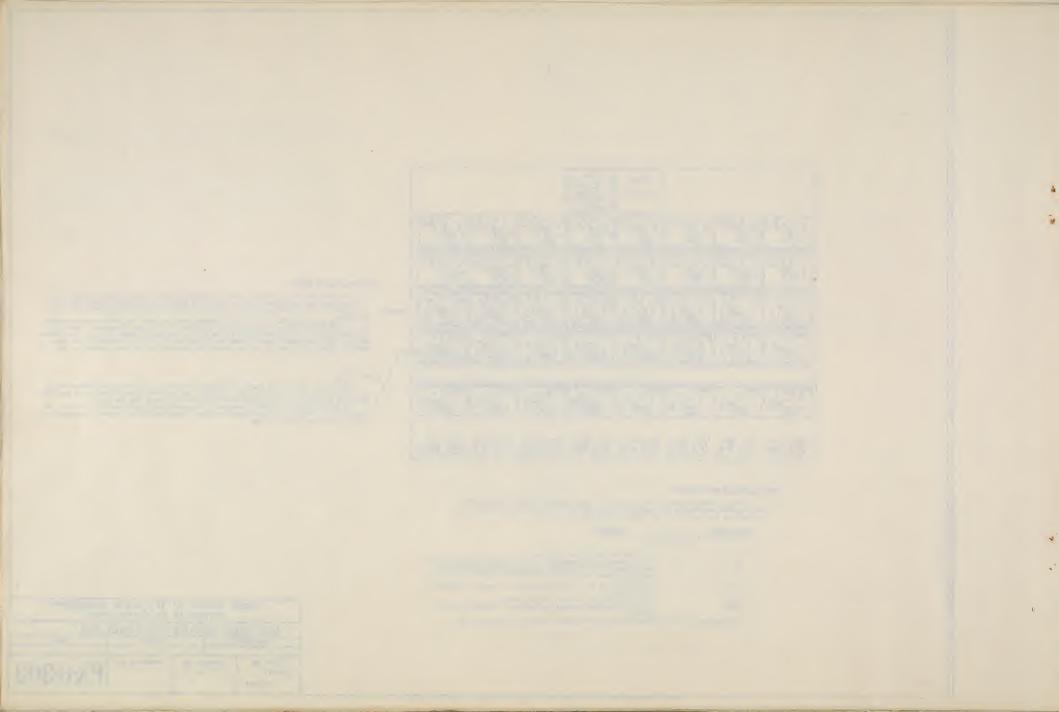MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA HIGH-SPEED MULTIPLIER FRONT PANEL NO.2 MATERIAL FINNSH SCOLE Drawn by: Charined by: Approved by: LEBELSKK OUT, MINING. DEC. 1944 PX-6-303



Important note concerning the partial products digit output terminals


These terminals are to be semi-permanently connected to the & digit input terminals (see note on terminals 1,r) of the product assumulators (#11, 12, 13, 14) by trays or cables not used for any other purpose. No load boxes are to be used. The digit pulses entited from these terminals are not supplied from transmitters, but from invorter tubes which cannot be connected in parallel with suppling else and which have their own resistors. Renoe the d digit input terminals of the product accumulators cannot be used for receiving eny other numbers.

No shifters or deleters are to be used. Accumulators 11 and 12 and accumulators 13 and 14 are paired when more than eight places is desired in the product.

The load on these outputs must be kept as small as possible. Recommended method of connection is;

L.H. #1 By special cable to accumulator 11. L.H. #2 By short cable to they (only one tray), and short cable to Accumulator 12. R.H. #1 By special cable to Accumulator 13.

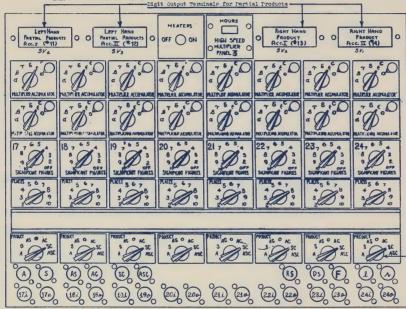R.H. # 2 Similar to I.H. #2 and Accumulator 12. See also drawing PX-6-311



Terminals A-ASC
Program output terminals associated respectively with A, S, AS, AC, SC, ASC, on product disposal switch.

Terminals RS, DS, F
Progrem pulse output terminals for transmitting pulses used in the programming of each multiplication:

DS - A program pulse is emitted at the end of the p+2d addition time if the multiplier is negative. Semi-permanent connections must be established so that this pulse programs the multiplicand acc. to transmit subtract and the right hand product accumulator I(#13) to receive.

RS - A program pulse is emitted et the end of the p+2d addition time if the multiplicand is negative. Semi-permanent connections must be established so that this pulse programs the multiplier acc. (#9) to transmit subtract and the left hand partial products acc. I (#11) to

F - A program pulse is emitted at the end of the p+3d addition time. Semi-permanent connections must be established so that this pulse programs the left hand pertial products accumulator (#11, 12) to transmit add (without shifting) and clear and programs the right hand product accumulator (#13, 14) to receive, or vice-versa.

Receiver cathode follower buffer output lines. These ere to be used to program the product ecc. to receive the partial products. The following semi-permanent connections are to be established.

- 1. I is to be connected via scc. interconnector cable (Mult.) (Pie-1-131) into the interconnector terminals I and I of left-hand partial products acc. I (#11). The digit input terminal is to be used to receive the partial products.
- 2. r is to be similarly connected into right-hand product accumulator I (#13). Likewise, the or digit input terminal is to be used to receive the partial products.

Product disposal switch


This switch operates in conjunction with program pulse output terminals A through ASC end provides program facilities for the disposal of all 24 products using at most 6 program controls of the right-hand product accumulator (#13, 14).


At the end of the p +4th addition time (i.s., at the same time as the program output pulse is emitted) a program pulse is emitted from A-ASC according to the setting of the product disposal switch of the program control being used.

Semi-permanent connections may be established by connecting A through ASC to six program pulse inputs of the right-hand product acc. (#13, 14) and setting the corresponding operation switches and clear-correct switches to transmit on A-ASC. The program control output pulse may he used to stimulate that unit of the ENIAC which is to receive the transmitted product.

DEC. 1944

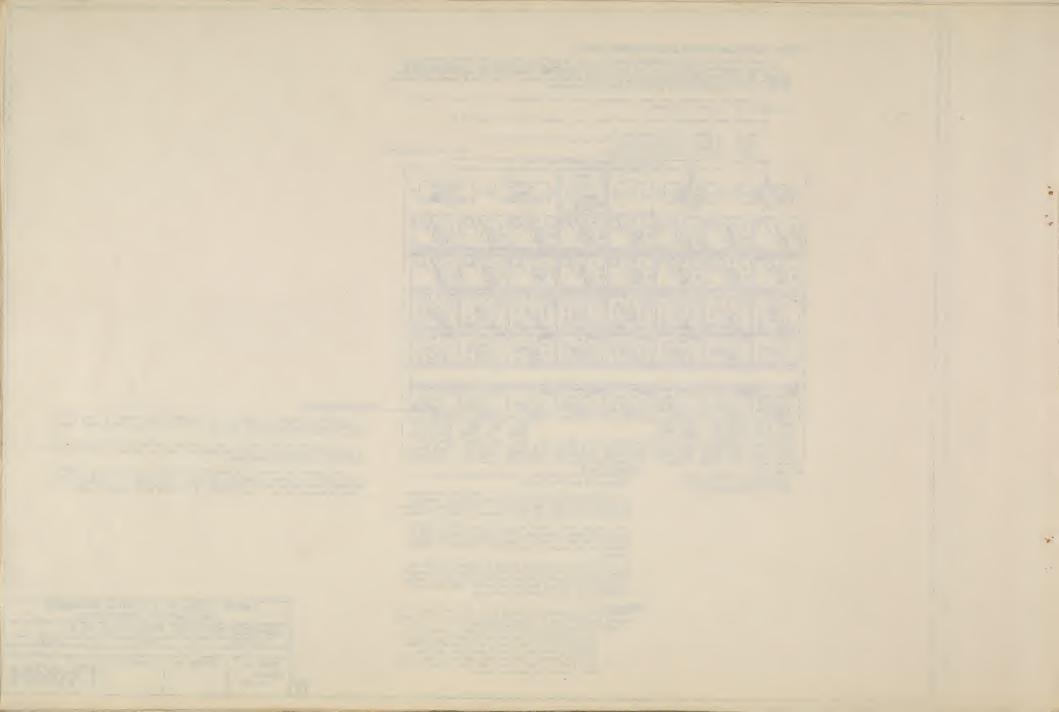MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA HIGH-SPEED MULTIPLIER FRONT PANEL NO. 3 MATERIAL FINISH SCALE LEBELSICK



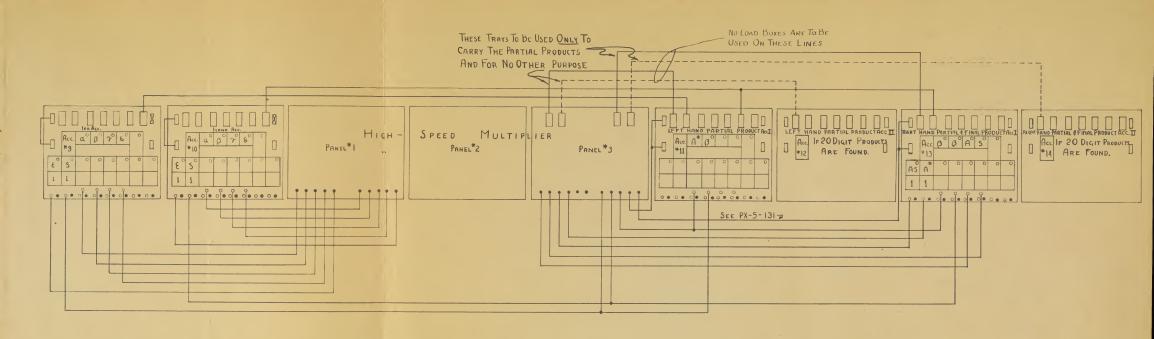

NOTE - HORIZONTAL LINES ABOVE THE UNITS REPRESENT DIGIT TRAYS.

THE DOTTED LINES REPRESENT TRAYS WHICH NEED BE USED ONLY WHEN 20 DIGIT PRODUCTS ARE FOUND.

MOORE SCHOOL FLECTRICAL ENGINEERING
UNIVERSITY OF PENNSLVANIA


INTERCONNECTION OF HIGH-SPEED MULTIPLIER WITH ASSOCIATED ACCUMULATORS ~ PX-6-311



Argument input terminal
This is open for reception of the two-digit argument during the 2nd addition
time of operation. The units place is received on line 1, the tens place on line 2,
Shifters [PC=1-04] should be used in this terminal to shift the argument if it comes
from other decedes than the 5th and oths. The other lines of this terminal are uncomnacted, so a deleter is not required.

The accumulator which transmits the argument may be programmed from terminals NC

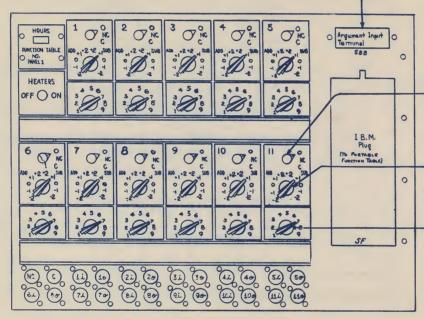and C. The function ...ole automatically clears its engagement at the end of each operation.



Terminals 11, 21,.....lli
Program pulse input terminals for program controls 1-11 respectively

Terminals 10 , 20 ,.....110
Program pulse output terminals for program controls 1-11 respectively

Program pulse output terminal associated with NC on ergument reception

Terminal C

Frogram pulse output terminal associated with C on argument reception switch.

There are eleven program controls on each function table. Each program control consists of a program pulse input hydright obstitute on sets induction the sets and program outrol consists of a program pulse input hydright of the program in the looking up of a function fall of the program pulse output farming (which a first pulse of the program pulse output farming (which a first pulse of completion of the operation), the three switches described below, and an essociated trunsceiver (for meon bulbs see PX=7=305).

Argument reception switch

This switch operates in conjunction with program pulse output terminals NC and 2 and may be used to program on accumulation or accumulations to transmit the argument.

At the end of the let addition the a program pulse is entitled from NC or 0 if this switch is

set on NC or C respectively. Semi-permenent connections may be established by connecting NC end C to program input terminals of the argument accumulator and setting the corresponding aperation switches to transmit and transmit-and clear respectively.

Operation switch

This switch determines whether the function value (add) or its complement (subtract) is trens-

mitted,

It also detarmines whether the function value of the argument received, or the function value of
one of the neighboring arguments, is transmitted. Thus positions-2, -1, 0, +1, +2 give f(a-2),
f(a-1), f(a), f(a+1), f(a+2) respectively, where a is the argument.

Operation repeat switch

This switch determines the number of times the function value is transmitted.

Note that A addition times are required for the function table to set up, receive the argument, etc. This loss of time must be taken account of in programming the accumulator which receives the value of the function. Thus if that accumulator is programms when the function. Thus if that accumulator is programms are the function. the function table with its repeat switch set to 9, it could receive the value of the function only 5 times.

Time Schedule for Function Table


Addition time Cperation


(Program input pulse received at end of Oth addition time)

- Circuits set up
- Argument received
 Argument modified by the addition of 0 to 4 pulses. At 14th pulse time portable function table starts
- Punction table finishes setting up
- Value of function transmitted
 This is continued up to the r+4th addition time, where
 r is the setting of the function repeat switch.

(Program output emitted at end of r+4th addition time)

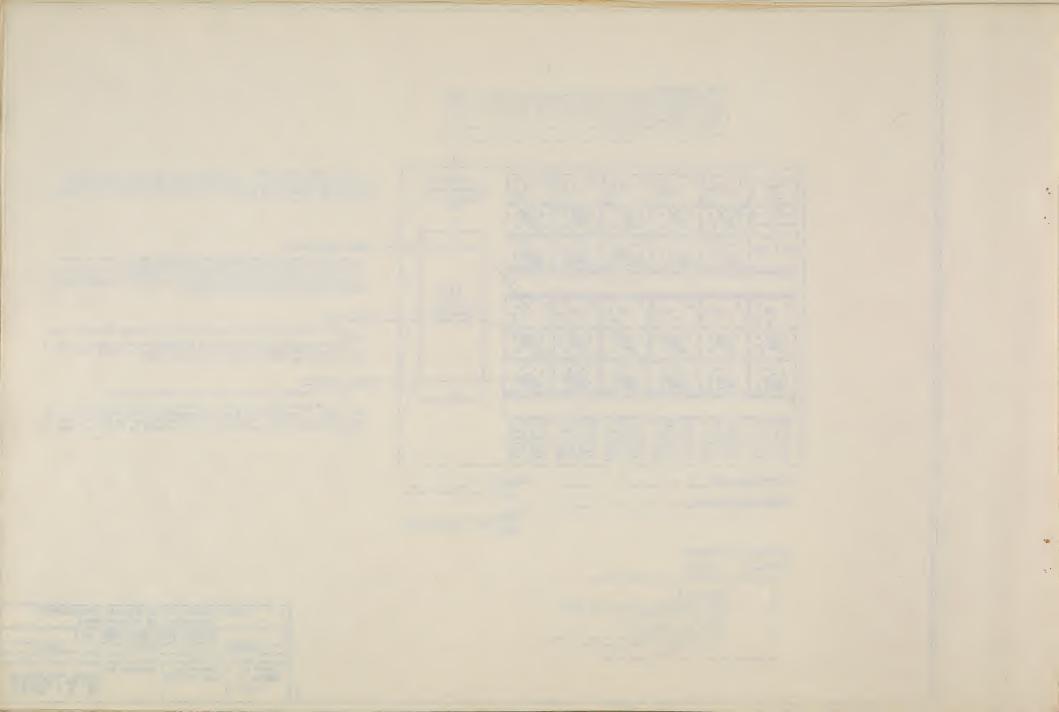MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA FUNCTION TABLE FRONT PANEL NO. 1 MATERIAL FINISH 2 4 1 20 Chained by: Approved by aws 10/25/45 TELETOKE PX-7-302



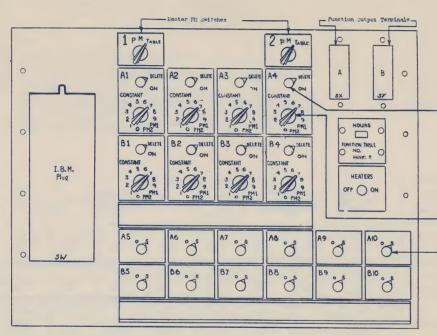

Sample row of switches on portable function table showing connection to function output terminals.



AMI Line 6 Line 5 Line 4 Line 3 Line 2 Line 1 Line 6 Line 5 Line 4 Line 3 Line 2 Line 1 TM2

For a positive number, set PM to P and set the number on the switches. For a negative number, set PM to M and set the complement of the number with respect to $10^{\rm M}$ on the switches.

Function output terminals
The digit ruless representing the value of the function are transmitted from these terminals. A
connection table appears helow. These terminals are to be connected to the digit trunks (trays) (see 1X=7-305) by the digit cables for transmission of the function value to another unit of the ENIAC. It is to be noted that the division of the eight constant digit switches and the 12 function table entries into the groups A and B was an arbitrary one, and by means of apacial adaptors (FX=0-110) those can be regrouped in any manner.

Table showing connections of function output terminals

Line	Terminal A	Terminal B
12 cround 11 PH 10 (Sillions place) 3 7 5 5 4 3 (Hundrede Place) 2 (Tens Place) 1 (Units Flace)	Oround Date of the second of t	Oround FM 22 Constant digit switch B3 Constant digit switch B3 Constant digit switch B3 Constant digit switch B4 Constant digit switch B4 Constant digit switch B1 Constant digit switch B1 Constant digit switch B1 Constant digit switch B1 Constant digit switch B2 Constant digit switch B2 Constant digit switch B3 Constant digit switch B4 Constant B4

- Digit dejets switch

Then the digit delete switch is set to delete the constant digit switch is disconnected from its

function output tesminal, otherwise it is left connected.


Digits which are constant for all the values of a function may be set up on the constant digit


If these switches are set to TMI or FMZ, the outputs of the corresponding master FM switches are fed through these switches to the output terminals. This feature is used when some of the left hand places of a function with both positive and negative values are zeros; these switches then supply zeros when the transmitted number is positive and nine's when the transmitted number is negative, thus avoiding the use of shifters at the receiving terminels.

Constant digit switch

On a subtract transmit these switches feed a subtract pulse onto their corresponding function output to winel lines if they are set to S. Thus the switch corresponding to the units digit of the function should be set to S; the others feeding onto the same digit trunk should be set to O.
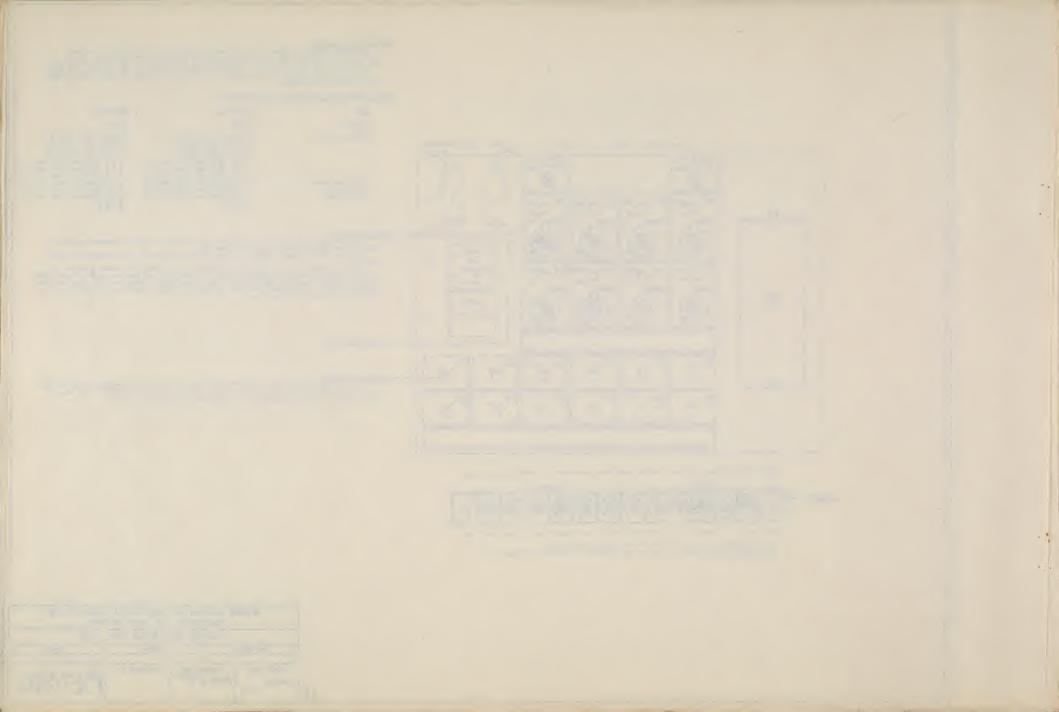
> MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA FUNCTION TABLE FRONT PANEL NO. 2 MATERIAL FINISH SCALE aws 1/6/45 J. EDELSACK



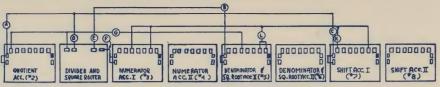

(In dividing the quotient is built up here. This acc. is not used in square-rooting.)

belong.

(The numerator or quantity to be sourre-rooted is to be placed

(In dividing the denominator is to be placed here. In square rooting twice the square root is built up here.)


Notes on cables:

Accumulator interconnector cable (quotient) (PX-5-134)
Acc. interconnector cable (denom.S.R.) (PX-5-136) digit tra ad box is used on a these nnections Acc. interconnector cable (shift) (PX=5-125)Stendard digit cable, with adepters (divider) (PX=1-114) plugged into program terminal. Standard digit cable, with adepters (divider) (PX=1-114) plugged into program terminal. Standard algat cante, with samplers (airlas) (pr. -- 11) plugged into program terminal. Acc. interconnector cells (divider) (pr. -- 227)

Trunk to transmit digit pulses for quotiert and aquare root.
This trunk is not to be used for any other purpose, since the pulses emitted are not supplied from truncmitters but from Inverter tubes which cannot be connected in perallel with anything clear, there inverters have their own load resistors, so no load box is to be used in connection

> (K) Standard digit trunk (with load box) using +1 shifter in of input of the shift accumulator. (L) Standard digit trunk transfer (with load box).

There are eight divider square rooter program controls, each consisting of a program pulse input terminal (which, when stimulated with a program pulse, causes the program control to program an operation, in eccordance with its switch settings), a program pulse output terminal (which emits a program pulse on complation of the operation, including interlocking) the eight switches described below, and an essociated transceiver (for meon bulbs see PX-10-302).

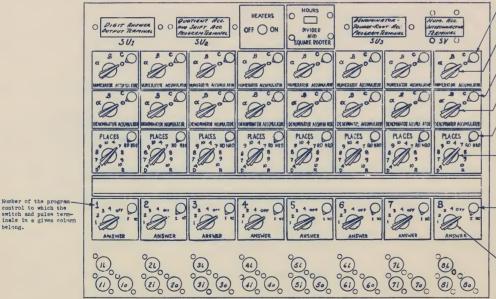

with its switch settings.

Terminals 11, 21,........ Interlock pulse input terminal,

If the interlock switch of a given program control is set at NI, these terminals are not used. If the interlock switch is set at I, a pulse must have been received on any interlock terminal since the last non-interlock operation or initial clearing of the divider before a program output pulse is emitted. The interlock pulse may be a program pulse or a digit pulse or pulses.

green pulse after both the operation is completed and an inverlock pulse is received (if interlock switch is set at I).

This governs the clearing of the remainder by means of the static cable running into the numerator accumulator PM plug-in unit. If this switch is set on C, the numerator accumulator is cleared of its remainder during the last addition time of the division or square root.

htmorator Accumulator Receive Satish
Then seni-paraments corrections are made, this switch programs the numerator accumulator to receive on the of and \$\frac{\pi}{2}\$ dight input terminals during the first addition time of the dividing or equere-rooting.

<u>Denominator-Square-Goot accumulator Clear Switch</u>
This switch operates the same as the numerator accumulator clear switch except that it governs the clearing of the denominator-square-root accumulator.

Denominator-Square-Root Accumulator Receive Switch

When semi-permanent connections are made, this switch programs the denominator end square root accumulator to receive on the of and \$\beta\$ digit input terminals during the first addition time of the dividing or square-rooting.

When set to Ro this switch causes the answer to be rounded off in the last place. Note: Even when the number (s) operated on are such as to give an exact answer this switch must be set to RO to give the correct answer.

Divide-Square-Root and Places Switch

This switch selects which process is carried out and the number of places (counting from the 10th decade, i.e. the highest place) of the answer.

Note: The digit answer output terminal is so wired that the answer is built up starting in the 9th decade (counting from the right). For ordinary operation the numerator (or number to be rooted) and denominator should be placed so that there is a 0 in the 10th decade of their accumulators. If the number to be rooted has en odd (even) number of places to the left of the decimal point it should be placed so that the left-hand digit is in an cod (even) numbered decade. Hence the answer will have at least one place less than the setting of the places switch.

Interlock Switch

This switch is used whenever another operation or set of operations is carried on simultaneously with the division or square-rooting.

An average division (in which there is a zero in the 10th decade of the answer accumulator) or square-rooting

takes 13p addition times, where p is the setting of the places switch.

If interlocking is used, and the interlock pulse arrives after the operation has been completed, a program output pulse in smitted during the second addition time following.

Answer Disposal Switch

This entith may be used to program transmission of the quotient or twice the squere-root during the first addition time following the completion of the operation. The program control output pulse will then be used to stimulate that unit of the ENIAC which is to receive the answer.

Positions 1 and 2 are normally used to govern the quotient accumulator. The operation they perform is deter-

mined by adapter (divider) (PX-4-114). Thus if PX-4-114A is used

Disposal 1 - Causes quotient ecc. to add transmit. Disposal 2 - Causes quotient acc. to add transmit and


clear. Similarly, positions 3 and 4 are normally used to govern the denominator-square-root secumulator.


MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA

DIVIDER AND SOUARE ROOTER FRONT PANEL

MATERIAL FINISH SCALE Drawn by Checked by aws 10/15/45 J. EDELSACK

DEC. 1944

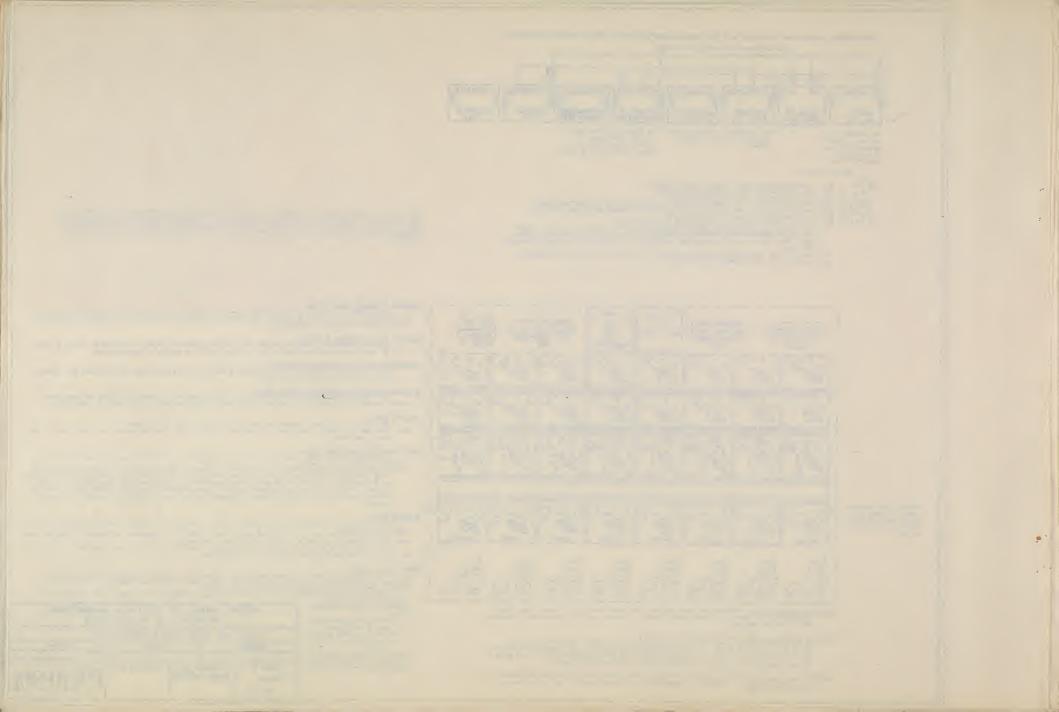

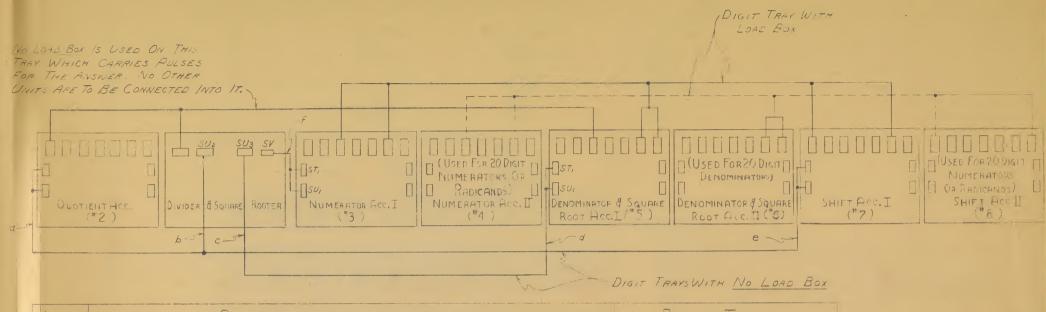

ITEM	DESCRIPTION	REFER TO
ST, SJ,	ACCUMULATOR INTERCONNECTOR TERMINALS	PX-5-105
SU2 } SU3 } SV }	DIVIDER & SQUARE ROOTER PROGRAMMING TERMINALS	PX-10-108
d	SPECIAL CABLE FROM DIGIT TRAY TO ST, & SU, OA QUOTIENT ACC.	PX-5-134
b }	ADAPTORS FROM SUZ TO DIGIT TRAY OR FROM SUZ TO DIGIT THAY	PX-4-114A, A & AC ADAPTOR PX-4-114B, A & S ADAPTOR PX-4-114C, AC & SC ADAPTOR
d	SPECIAL CABLE FROM DIGIT TRAY TO STI & SUI ON THE DENOM. & SQ. ROOT ACC.	PX-5-136
l	SPECIAL CABLE FROM DIGIT TRAY TO STI & SUI ON THE SHIFT ACC.	PX-5-135
F	SPECIAL CABLE FROM SV TO ST, \$ SU, ON THE NUMERATOR ACC.	PX-5-132

MARE SCHOOLS ELECTRICAL ENGINEERING

INTERPONDENT ON CE DIVICENTISO HER BOTH WITH FORESTEN HEROLOMULTURES - PX-10-307




Memower the transmission of a constant is programmed digit pulses representing this constant are emitted from this terminal. This terminal is to be connected to a digit trunk (fray) [One PA-IL-906] by a digit cable for transmission of the content to another unit of the IMAGA.

A table showing the connecting of this terminal for left-hand and right-hand five digit group, and combined loft and right-hand ten digit sets, appears below.

It should be noted that a left-hand five-digit group would be received in the left-hand half of an accumulator and a right-hand five-digit group would be received in the left-hand half of an accumulator and a right-hand five-digit group would be received in the left-hand half of an accumulator and a right-hand five-digit group would be received in the left-hand half of an accumulator. the right-hand half if no shifter were used.

Line	10-digit number (LN)	5-digit left-hand number (L)	5-digit right-hand number (R)
12 11 10 9 2 7 6 5 1	Fround PM (of L) Billions place Humiruds place Tens place Unite place	Ground FM. (of L) Ten-thousandths place Tens place Unite place Rothing Nothing Nothing Nothing Nothing	Ground FM (of R) FM' (of R) Ton-thouseniths place Unite place Unite place

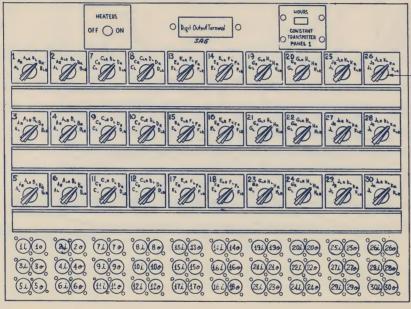"Thus o pulses are transmitted on these lines when the constant is positive, 9 pulses when it is a complement. Hence it is unnecessary to use a shifter on a receiving accumulator to receive this constant into the units to ten-thousands decades of that accumulator.



Terminals 11, 21,.... 301
Program pulse input terminals for program controls 1-30

Terminals 1 , 2 ,......30
Program pulse output terminals for program controls 1-30

Constant selector switch

General Explanation of the Constant Transmitter

The constant transmitter her a capacity of 100 digits and 20 signs. These are divided into 10 sets (A,S,....3, J,K) sech consisting of 10 digits and 2 signs, Zight of these sets (A,S,....) are sumplied from IRI contact knows the IRE reader when proper connections are made on the IRE reader plug board (see PX-11-305). Two of thuse sets (J, X) ere supplied from the constant set switches and PM set switches of

penel 2 (see Ex.11-03); her divided into two groups, a left-hand group and a right-hand group, each consisting of 5 digits and a sign. This division must remain fixed throughout a given set-up. For example, if the c set is divided into five-digit groups, then any or all of the constant melactor switches 7 to 12 may be set to C, or C, but not to Cr... Conversely, if the E set is not divided, then may or all of the constant selector switches 13 to 15 may be set to E, Dut not to E, or A...
The HE resider is programmed from the initiating unit (see FA-9-302). The HEM reader controls and

plus-board are described on PX-11-305.


Constant Transmitter Program Controls


There are 30 constant transmitter program controls, each capable of transmitting certain of the constants over the digit output terminal. Only one program control can be used at a time, hence only one number can be transmitted at a time. Fach program control consists of


- Program pulse input terminel (when stimulated with program pulse causes program control to program transmission of number set on its constant selector switch)
- 3) Frogram pulse output terminal (emits program pulse after constant has been transmitted, i.e., one addition
- time after the program pulse input terminal has received a pulse.

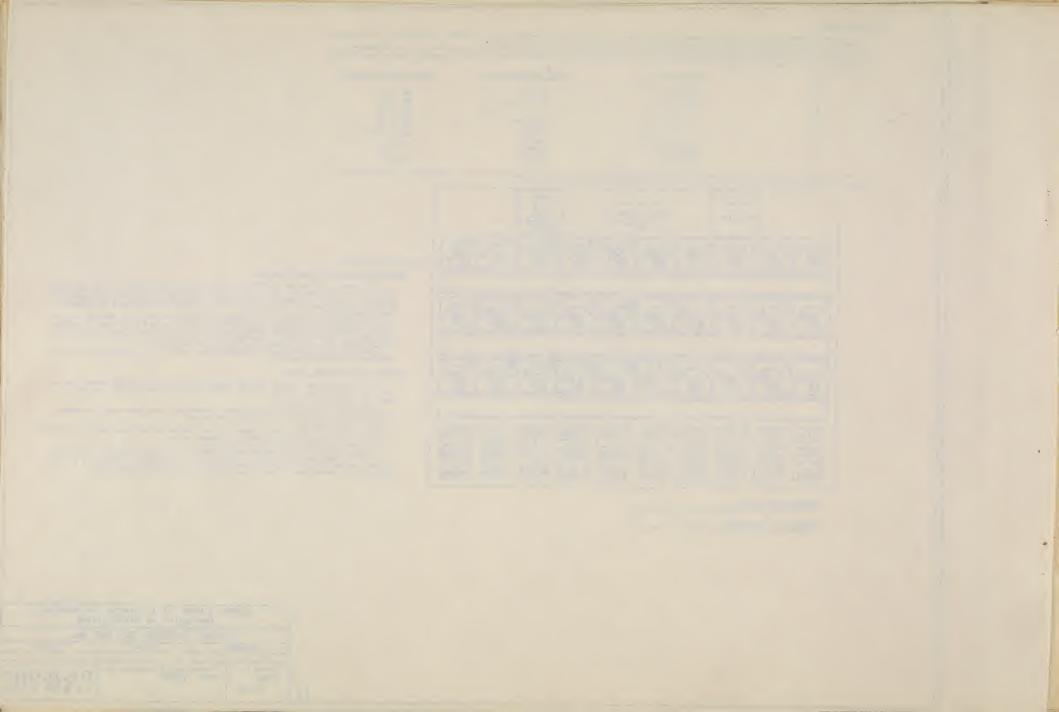
 4) Associated transceiver (for mean bulbs see PX-11-306)
- Program controls 1-24, which treasmit constants read from the IEK cerds, cannot be used during the operation of the eard reader, except during the first 50 addition times of this operation. That is, efter a pulse is supplied to Ri on the initiating unit from panel (see PK-9-302), these control may be used during the 50 subsequent addition times, but not thereafter until e pulse is emitted from Ro.


MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA CONSTANT TRANSMITTER FRONT PANEL NO.1 MATERIAL FINISH SCALE JUT 1/1/45 Drawn by: Approved by LEDELSAKK



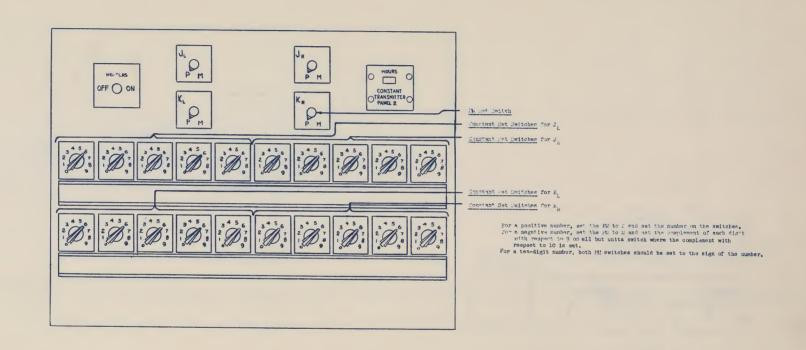

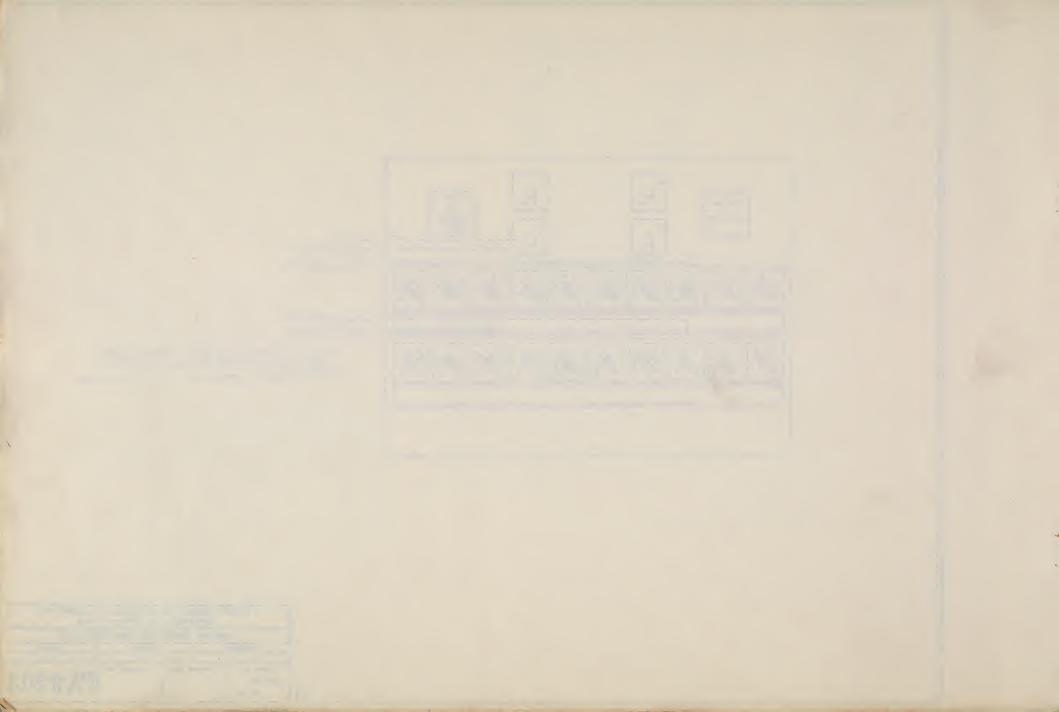


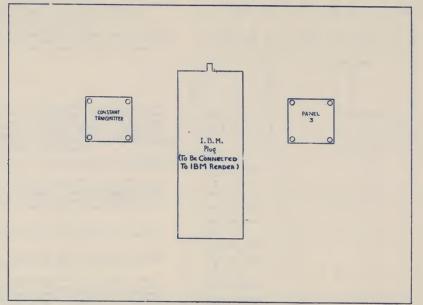

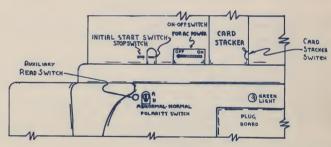

Note: Do not change polarity switch while motor-generator is on.

	MOOR			ELECTRICAL OF PENNSYLV	
	(CONSTANT	TRANSP	TITTER FRONT PAN	IEL NO.3
+	MATERIAL			FINISH	SCOLE 3
	DEC. 1944	Check	o oy:	Approvid by:	PX-11-304

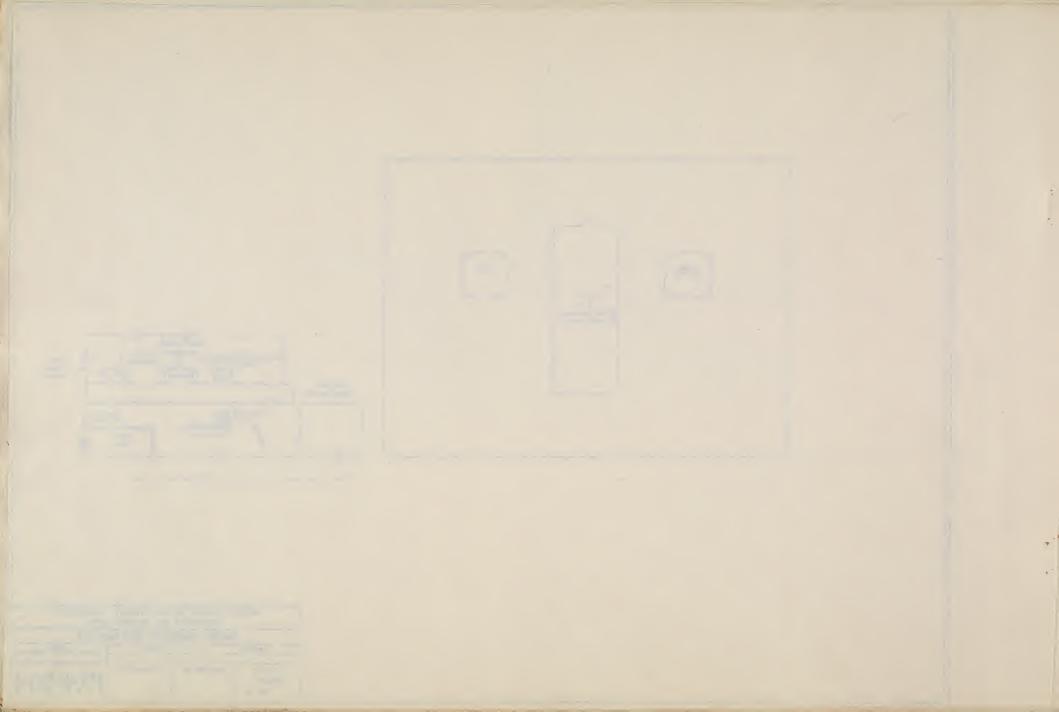

The Polarity Switch

Located on the front of the IRM Reader is a double pole double throw switch which changes the polarity on the holding coils of the relays which control the group selection and the reset control. By planning this switch one onn either wire these circuits on the plug board in the manner indicated there or in the rewerse manner. This gives the following types of control.

(B) With the polarity switch in sonormal position, In this case "O" is wred to some digit on the digit selector and the group selection bubs are wired to vertious columns. Here, all the control is obtained by a certain punch (for example, a 12 punch) with different things being controlled by plugging to different oclumns.

Plugging Illustrations

- .(a) This shows the common hub "C" wired to column 21. The two hubs above and below C are connected so the wire could have gone to either of them. Note that besides the wire (a) one could connect this upper hub for C to some other column, say 2, getting an "or" control. That is, if a certain number (12, 11, 0,...,9) is punched in column 21 or column 2 then whatever hub under group selection was plugged to that number of the digit selector causes the corresponding group selection relays to operate.
- (b) This wire causes the reset control to operate whenever there is a 12 punch in column 21; that is, a card with such a punch is called a master card.
- [c end d] These leads cause information in storage relay groups 6 and 7 to be held as long as cards come through without a 12 punch in column 21. Thenever a card with a 12 punch in column 21 (a mester card) comes along the information in groups 6 and 7 will be dropped and new information will be put in from this mester card, Immediately, the reader will go on to read the next card,
- (c) If a card has a 6 punched in column 21 this lead causes group selection relays for group 12 to be activated giving a circuit from C through B instead of A.
- (f and g) If a 9 is punched in column 21 groups 15 and 16 group selection relays will be activated. Diagonal leads such as (f) enable one to operate as many groups as desired from just one punch.
- (h, j, and K) This shows the plugging to bendle ten digit negative numbers. The FM punch is in column 1 and, by the diagonal connection in the minus control, the FM relays for groups 1 and 2 are operated by this one punch. The first digit receive the storage relays through (j), (k) illustrates the plugging for the rest of the digits.
- (n, o, end p) If there is a 6 punch in column 21 the digit from column 20 will go to the fifth digit of group 8. Otherwise, the digit from column 40 will go there.
- (m, q, and r) If there is a 9 punch in column 21 the digit in column 80 will be the fifth digit of group 12. Otherwise, it will be the fifth digit of group 16.

NOTE: If during the course of a computation the IBM reader should run out of cards the starting relay (see FX-11-307) will be closed so the moment new cards are dropped in, the reader will go through a cycle. To make sure that the reader does not fail to feed this first eard the stop button should be held down until the cards are firmly in place.

		-	-																	mass - ~				-				Q
			0	0		0	- 5			0	0	-#1	Read	Brue	hes			15	-					- 20				
			•	٠	۰	•	25	,	•	٠	·	۰	30	0	0	, ,	• •	35	(,	0	0	0	40				
		+	0	0	0	0	0		0	0	0	0	0	0	c		0	0)	0	0	0	0				
			0	•	0	0	45		,	0	0	0	50	0	c			55			٥			60				
	a		•	•	۰	,	65	,	•	•	•	•	70	0	0		0	75	,	,	۰	•	0	80				
			0	0	. 0	0	0			0	0	٥	0	0	C			0			0	0	0	0				
			PL t	01	RB		g to		88	0	0	0	7 0	0	- G1		elect				0			_				н
		4	-		Ġ		/b i	- 1	2	3	4	5	6	7	8						13	14	15	16	1			
			0	0	0		0		•	0	0	0/	0	0		0	, ,			20	0	0	0	0	18			
			0	0	- R		shunt		0	0	0	12	- 11	0			git e	elect		-/	6 -	- 7 -	- g	- 9	1			
		1	Ī	Ĭ	Ĭ	- 1	Ĭ		Ĭ	ĭ	Ĭ	-								,	-		-5					
			ė .	0	d		Ó	×.0"	9	0 1	۵	0	0	0	(•		0)	0	0	0	0				
			PL t	20	set 30					70	go	Rea 90		ntrol 110		130	140	150	16		0							
		ď					,,,			10		70	100	110	120	, 15	170	190	10	_	o	0	0	0				
			0	0	o				0	0	D	0	0	0	1					3	9	0	0	9				
			0		0		5		0	0	0	#2 H	ead I	3rushe	8			15		0	0			- 20				
		1	~	Ar .	,	,	25			٠	0		30	٥	,	,	,	35		3	٥	0	0	40				
	fr	1	9/	0	0		0		0	0	0	0	0	0		9	٠ (9		0	0	0	0	a				
	l.	4	0				45		0	0	0	٥	50					55						60		1		
	X			۰	,	, ,	65		U	0	0		70	•	,	•	9 (75		0	0	0	0	80		1	1	
(/ \	1	0	0			9		0	0	0	0	0	0		0	0			0	0	0	0	0,		1		١,
١		7	Plue	a to	RB				0	0	0	N	inua	contr	01	-	0			0	(D)		0	'	1			(
1			1/	100	3				6	7	đ	9	10	11	11						(10)	٥	0	0				
١		-	8	0	-				0	0	0	o	0	0				0		0	0	0	0	0				
			/	0		, ,	, ,		0	0	0	0	0	0		0	0				0	0						
ı	1	1	Plu				-		-	0				select					,	0	0	_ ¥ .	0	0	l i			
١			0 6	0					0 (0	0	0	0	0	G	0	0	,	•	o C	0	0	0	0				
			Plu			rela			o &	0	0	0	٥		A	0	0 (, ,		o &	0	۰	0		m	n		
1						rela		'		٠.	٠	٥	۰	"	A	u		, ('	0 26	0		0	۰	m	11	0	1
1			0 3						o B	0	0	0	0	0	B (0				0 1	0	0	•	0				
1		il	Plu						o C	0	0	- 6	0	-	0	0		7	. +	0 0	0	g -	0	-				
1		1				rela	78			•	•	٠	٠	"	•	•			1		٠	٠	·	۰				
1			OA	. 0) (•	0 A	0	0	0	0	0	A	0	0	9 (•	0 A	0	0	٥	0				
١			o B			rela	/8) (.	о В	0	0				В	_	0			о В	_	0	0	0				
1	- 1		Plu	g to	21		-	-				- 10	_	-			1		-	0 1		- 12 -				/)	
		1	0 0					•	0 0	0	0	0	0	0	C ·	0	0	0		o C	0	0	0	٥				
1			O A			rela	78) (,	o A		0	٥	0		A	0	0			0 A	•	0	0	ď	N			
			Plu	z to	ST	rela					Ŭ	·	Ŭ					,	1		0	•	٠	۰	M	1		
			0 1				,	·	o B	0	0	0	0	0	В	0		9 (o B	0	0	0	ď	1/	'	1	
1			Plu	t to	21	CB			0 0		0	14	0		C		1	9	, +	o C	0	- 16 - o	0	0	X			
						rela					٠	·	٠	"				•	'		0	٠		0				
1			o A					·	o A	. 0	0	0	0	0	A	0	0	0	9	o A	0	0	0	0			P	
			o B	g to		rela	/8) (, I	о В		0	0	٥	١,	В		0			o B		٥	۰	Q.			1	
	\vee		• "			•	•	•			•	٠	Ŭ	٠	2	•			,	0 2		٠	٠	ď	1	1		,
		4	0	0			•)	0	0	0	0	0	.0		0'	0	0	•	0	0	0	0	0	2		/	
		1	8	Or	oup				0	0	0	- Sto	egero o	Relay		0	0	0 (0	- Gr	oup 4	0	0	1			
			·	- Gr	oup			-	_		oup 6	_	0	0		o Group			-			oup a	- 0		V	q		
			9	0		0 (•		0	0	0	٥	0	0		0	0	9 (0	0	0	0	۰	or or	1)	()		
			0	- (37	quo		,		0	- Gra	oup 1	0	0	0		Group o		0 4	,	0	- Gr	oup 1	2	~	X.	/		
					oup			4	_		oup 1			- 0		o Group			_	·		oup 1			/			
		-	0	0	-	0 (5	0	0	0	0	0	0				0 (,	0	0	0	0	ď	3			

#1 Reed Brushes

The #1 Reed Brushes reed the card before the #2 Reed Brushes do. The #1 brushes are used for control purposes and the #2 brushes for reading the numbers and their PM's.

Group Selection

The hubs numbered from one to sixteen control the group selection releve whose terminals are located on the lower haif of the plig board. These are double hubs, that is, the hub above and below the number are common, the single hub located to the left of these and labeled RG control the reset control. The features of group selection and reset control are described below, For details see the IBM reader wiring discrame FV-11-119.

Reset Control and Reset Shunt

Cartain groups of relays (depending upon plug board errangement) may be ounced to hold their information while a sequence of "detail" cards are read. This is accomplished by connecting the corresponding terminals under Reset Control to eny of the Reset Shunt terminals, To change the information which is being held in these relays a "master" card is inserted in the sequence of cards. A particular punch on this master card can cause the held information to drop out and as the master card passes the \$2 Reading Bruches new information can be stored in these relays until the maxt master card comes along. Whenever such a master card is read the Reader will immediately read the next detail card before it gives out a computing signed to the RNIAC.

MARNING: The detail cards either must not contain information in the fields corresponding to the relays that ears holding master card information or else group selection must be used to prevent such information for midsturping the held relays.

Group Selection Releys

There are sixteen five pole double throw relay switches, called the group selection relays. The common terminale are labeled "G" and normally the circuit is through the terminale labeled "A". When cattwide (picked up) the circuit is through "B". These circuits are isolated (intermally) from the other circuits of the reader so there are many other possible plugging arrangements other than those indicated on the plug board,

Minus Control

By meens of came in the Reader these terminals connect to the PM relays of the Constant Transmitter only when the IBM cerd is in positions 11 and 12, that is, when the PM punches would be under the #2 Read Brushes. The two hubs. above and below the group number, ere common. Usually, the punch for minus indication will occur in the same column that digit punch appears. Thus, the same reeding brush will indicate the PM of the number and leter as the positions zero to nine pass under the brush indicate the digit punched. Other cams (called coding cams) energize the numerical circuits only during the zero to nine part of the cycle enabling the digit punch in that column to cause the proper relays to be set up in the Constant Trensmitter. The coding cams consist of two groups, one group is used for positive numbers and the other group causes complements (with respect to 10 -1) to be set up by storage relays. The PM relays determine which set of coding cams are used.

Storage Relays

The storage relays are located in the Constant Transmitter, there are sesentially four relays associated with each digit. That is, four relays representing respectively 1, 2, 2, 4, 6 cm, in various combinations, represent any digit from zero to nine. These four relays are indirectly (through vacuum tube circuits) essociated with the 1, 2, 2, and 1 pulses sent out by the cycling unit. That is, each relay opens a gate tube which through an inverse opens a second gate tube. This second gate tube passes the 1, 2, 2, or 1 pulses.

For postire numbers the nuls of the \$2\$ reading brushes

For positive numbers the hubs of the \$2 reading brushes can be wired directly to the hubs of the storage releys in any order whetecever. Negative numbers must be handled in groups which are multiples of five. To indicate the negative number there will be en 11 or 12 punch in some column. The wire from the hub representing this column must go to the minus control hubs of all the storage reley groups used for this negative number. There must also be a connection to the hub corresponding to this digit in the storage releys. See the exemples shown to the left.

MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA

FINISH

1. B. M. READER PLUG BOARD


J. Cummings Aug 4, 1945 12-7-45


MATERIAL

Approved by:

PX-11-305

SCALE

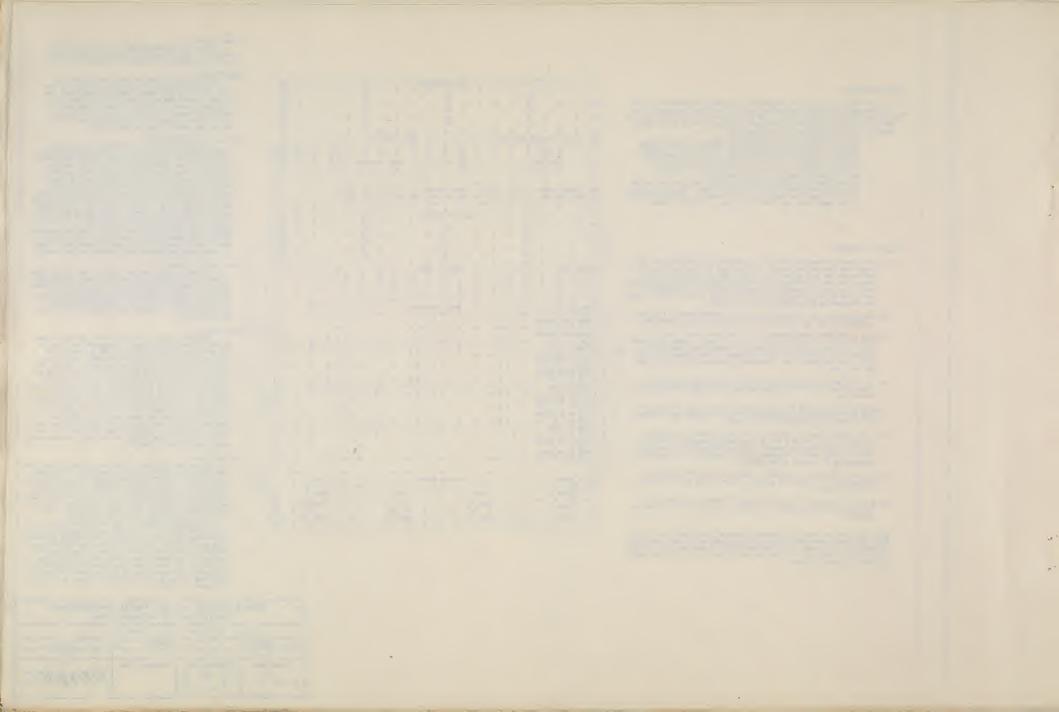

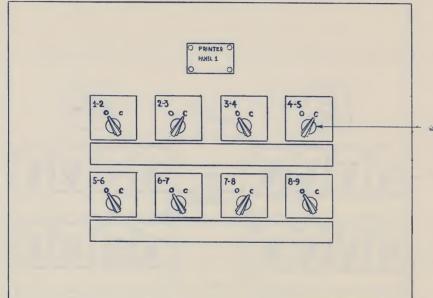


Coupling meitch


This switch roughes two groups of digite together when it is set to the C position. It provides for the retryover when an NHLN complement is converted to a true value.
The switches or this drawing and Y-(12-37) arm set for the primagement shown in the table below.

Table Phowing Original Sat of Decades Connected to the Printer

Decades from
Moster Programmer, Fenel 1, Deceder 14-18
Accumulator 13, Decades 6-10
Accumulator 13, Decades 1-5
Accumulator 14, Pacades 6-10
Accumulator 14, Decades 1-5
Accumulator 15, Decades 6-10
Accumulator 16, Decades 6-10
Accumulator 16, Decades 1-5
Accumulator 17, Decades 6-10
Accumulator 17, Decades 1-5
Accumulator 18, Decades 6-10
Accumulator 18, Decedes 1-5
Accumulator 19, Decades 6-10
Accumulator 19, Decades 1-5
Accumulator 20, Decedes 6-10
Accumulator 20, Decades 1-5

İ	MOOR	UNIV	ERSITY	ELECTRICAL OF PENASSEL	
F	MATERIA.			SINICH	
	Drawn by: U-EDELSACK DEC-1944	Check dup	10/21/45	Approved by:	PX-12-301

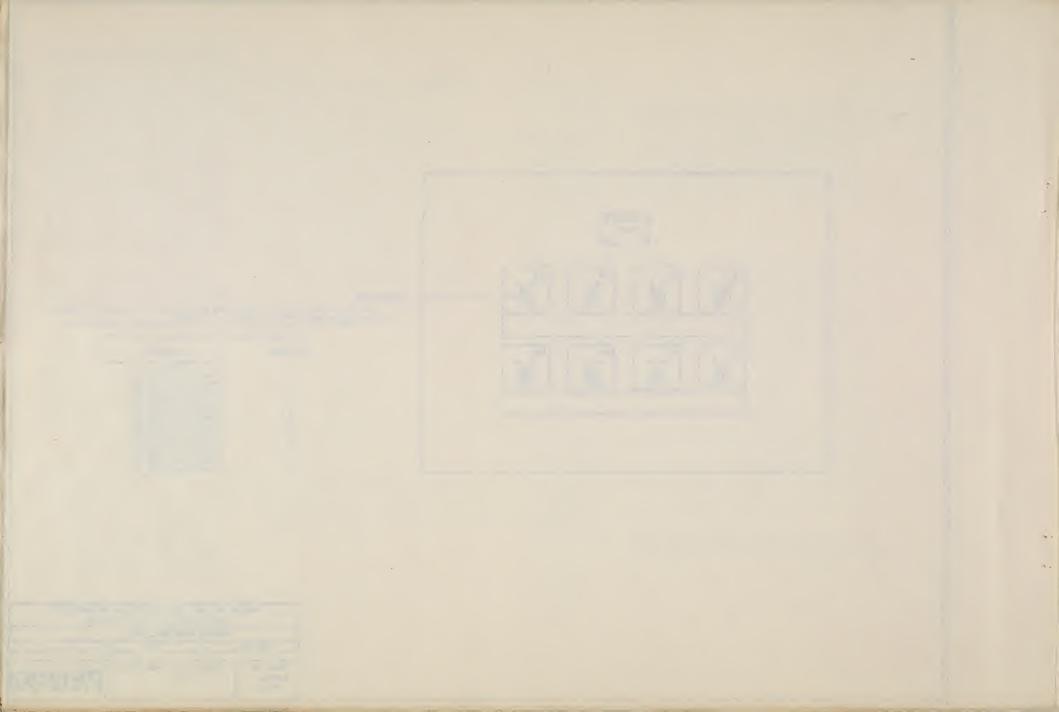

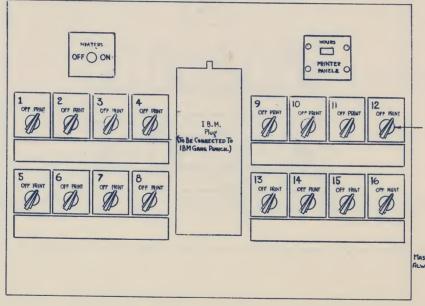

General Explanation of Printer

The printer operates from the static outputs of accumulator and master progresser decades. The cables connecting the decade static terminals to the printer lie in a trough at the top of the front of the machine. A table, showing the original set of connections, appears on PX-12-301. Every accumulator decade and PM unit and every master programmer decade has a static output term-

Every accumulator decade and FL unit and every measure programs.

The numbered to be printed are divided into eixteen groups of 5 digits and a FM, numbered from 1 to 10. The printing switches determine which groups are connected to the IBM gang purch. Drawing FK-12-905 shows the IBM gang purch plug board and gives instructions for connecting it up.

Any group of five digits and a FM may be connected to an adjacent group by means of the coupling switch, so that 10 digit, 15 digit, etc. numbers may be punched.

Elent the number to be printed in a complement (i.e., the FM counter registers M), the true value of the number is numbed along with an 11 punch to indicate that it is negative.


So the number is numbed along with an 11 punch to indicate that it is negative.


Theorems into the insurer is pursue along with our is purent to indices that it is negative.


Therever into the interior in the smater programmer is printed deptor PX-12-114 B must be used at the printer place on panel 2 so as to ground the unused IM lead going into the printer.


The printer is programmed from the intitiating unit (see Ex-9-502). Outstoll on the IEM garg punch ere explained on PX-12-305.

This switch connects (in the "Print" position) or disconnects (in the "off" position) the voltage supply to the buffer tubes of its group, so that these tubes do (or do not) operate the relays when the printer is pro-marmed. For the group of digits to be punched it is necessary not only that this switch be set to graint" but also that proper connections be made on the IEM gane punch plug board (see DA-12-305). This switch must be turned off if the decades to which the group is connected ere not turned on.

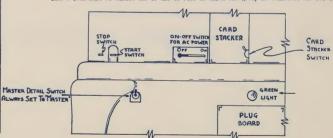

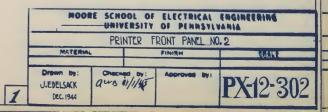

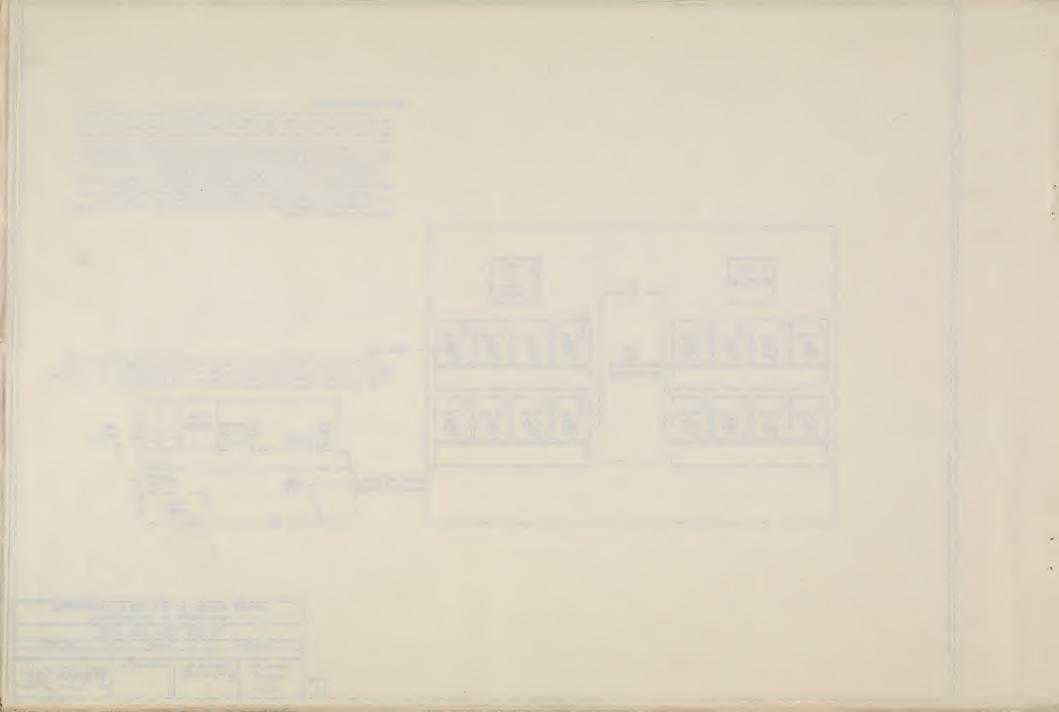

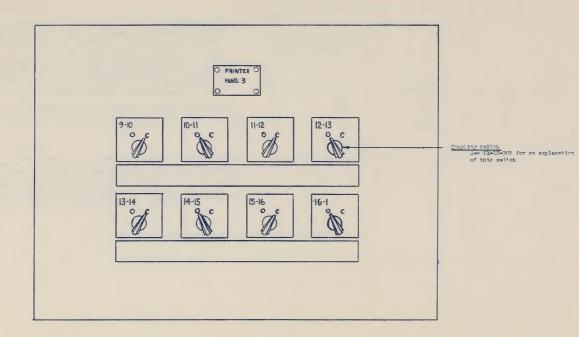

MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA

PRINTER FRONT PANEL NO.3


MATERIAL SINIEM

Drawn by:

Checked on:

Addroved by:

PX-12-303

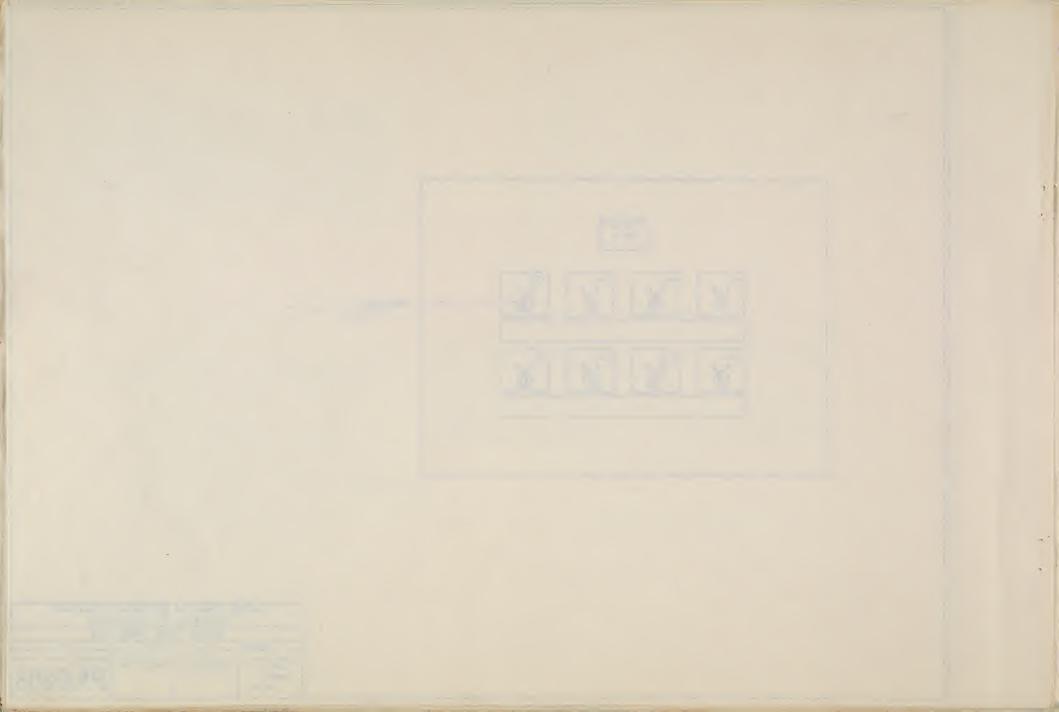

PIUG BOARD FOR GANG PURCH

Computer Result Exit

These hubs connect directly to the digit relays in the printer. To punch positive numbers they can be plugged to the punch megnet hubs in any desired errengement. Thus, it is possible to place the digits coming from the group 1 relays in any five of the eighty columns on the ITM

Minus Indication.

The sixteen hubs under minus indication go directly to the PM releys of the sixteen groups. The minus indication of any group could be punched in any of eighty columns on the card simply by connecting the corresponding minus indication hub with the particular column hub of the punch magnets.

Usually, however, the minus indication will appear above some digit of the number on the card. To place the minus indication (an Il punch) above the first digit of the number the minus indication of the corresponding group is plugged to one of the terminals labeled "A" under column splits. The hubs "my and "o" directly under the A-mbu used are to be plugged, respectively, to the digit hub (Computer Results Exit) above which the minus punch is desired and to the corresponding hub of the punch magnets.

The column splits is simply a sixteen pole double throw relay switch. This switch is controlled by a cam in the IEM punch which causes the "g" hubs to be connected to the respective "A" hubs during the 11 position of the card and to the "B" hubs during the 0,....,9 position of the card.

Fmitter Outputs

If one of these hube is plugged to a punch regnet hub the corresponding number will be punched in that column of the card, the five rows of five common hubs to the right of the emitter outputs enable one to punch the same number in more than three columns. The connection labeled (e) on the diagram causes nines to be punched in the columns 77,...,50 on the cerd, Connections such as these cause the corresponding number to be punched in every card. This can be used to give identifying numbers to the cards or to punch dates on the cards. Alphabetic punching cannot be done on this medium.

		F	- Or	oup 1					Com		Do au	lt Exi								_	
		P	<u>_</u> 0	0	0	0	0	0	0	0	O O	O	0	0	0	0	0		roup	-	- 0
	/	0		oup 5	0		+		oup 6				Grou	p 7	-		-	_ G	roup	.	
]	-	o oup 9	- 0	٥	0	o Gr	oup 1	0 -	0	0	Grou	0 11	0	0	0	0	roup :	0	0
/		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
		0	- Gr	oup 1	9	0	0	Gr	oup 1	.4	0	0	Grou						roup :		-
	I										0		0	0	0	0	0	0	0	0	٥
	d	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	1		. 8 -		u i	nus	Indica	tion			- 10 -	- 11	12 -	13 -	- 14 -	- 15	- 16 -	7	·	·	·
	P	DL 1	to Mi	o nus Tr	o nd	0	0	o column	O Spli	0	0	0	0	0	0	0	0		0	0	0
	\ `	O A	. 0	0	0	0	0	0	0	0	0	0	0	0	0	0	0		0	0	0
		PL 1	to Cne	o o	r Res	ult !		0	٥												
			o Pui				٥	0	0	٥	٥	0	0	0	٥	0	0	0	0	0	0
	/	40 C		0	0	0	0	0	0	0	0	0	0	0	٥	- 0	0	0	0	0	0
_		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0		0		
1	C				-						Ů		v	0		U	U	0	0	0	0
		0	0	0	0	, o , 5 -	0	0	0	O	o h Mag	0	0	0	0	0	0	0	0	0	0
		0	0	0	ъ	~ ŋ -	0	0	0	Punc	n Mag	nets	0	0	0	- 15 0	0	0	0	0	20
						25					30					35					40
		0	0	0	0	45	0	0	0	0	o 50	0	0	0	0	0	0	0	0	0	60
		0	0	0	0	0	0	0	0	0	0	0	0	0	0	55 o	0	0	0	0	00
		0		0	0	65	0	0	0		70					75					50
			_				Outpu			0		0	0	0	0	0	0	?	P	P	?
		9 "	9	٩	P	P	P	٩	٩	٩	P	0	0	0	0	0	p	- 8	-6	-6	_1
		12	611	00	01	62	93	04	05	06	97	08	69	0	0	0 /	/	- 0-			
		i				1				- 1		-	1/-	0	,						
		0	٥	6	0	٥	ò	6	ъ	6	ь	0	3	0	, 0	0.	0	0		-0-	0
		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0				0
		٩	0	0	0	0		0	0	0											
		. "	٥	U	9	0	9	0	g	0	0	0	0	0	۰	0	0	0 -	-0		0
		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	9	0	0	0
		ð	0	0	0	0		0	0	D	0		0	0	0	0					
	- 1											· ·	٠	0		U	0	0	0	0	0
	-	9	0	0	0	0	0	0	9	9	ο.	0	0	0	0	0	0	0	o	0	9
	i	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	٥	0
															-	-					
		0	0	•	0 '	0	0	0	0	0	.0.	0	0	0	0	0	0	0	0	0	0
		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
		0	a	0	٥	0		•													
		-	,	,	J	0	0	0	0	0	0	. 0	0	0	0	0	0	0	0	0	0
		b	9	٥	٥	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
		0	0	0	0	0	0	0	0	ъ	0	0	0	0	0	0	0	0	0	0	
					-		-	-					•	,	,		0	0	0	0	0
		0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
		0	0	0	0	0	0	ó	0	0	0	0	0	0	0	0	0	0	0	0	0
																		-			- 1
		0	0	0	0	. 0	• ,	0	0	9	0	0	0	0	0	0	0	0	0	0	0
		0	0	o	0	0	0	0	0	0	0	0	0	0	0	0	о	0	0	0	0
																					. 1

Plugging Illustrations


- (a) This illustrates the type of plugging in columns where no minus indication is desired.
- (b, c, and d) When the 11 position of the card is under the punches there is a connection through leads (c) and (d) from the punch magnet hub to the minus indication. If the group 1 FM relays were activated a signal will arrive at this time causing the 11 to be punched in column 1 on the card, if the 11 punch indicating a negative number were desired in column 2 leads (a) and (c) must be interchanged at the punch magnet hube and leads (a) and (d) interchanged at the computer exit tube. Then the first column of the computer exit comes directly to the first column punch and the second column leads go through the minus indication hube and the column split.
- (e) These connections will cause nines to be punched in the lest four columns on the card.


MOORE SCHOOL OF ELECTRICAL ENGINEERING UNIVERSITY OF PENNSYLVANIA

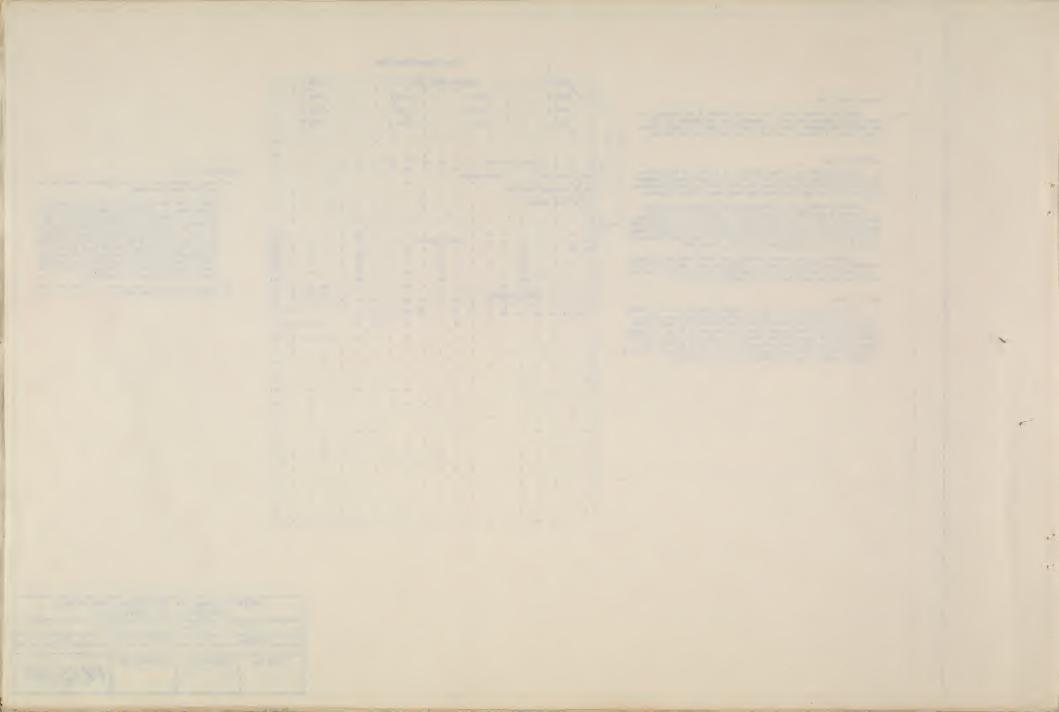1.B.M. GHANG PUNCH 1240 BORRD

MATERIAL FINISH SCALE

Drawn by: Chapter by: Approved by: PX-12-305



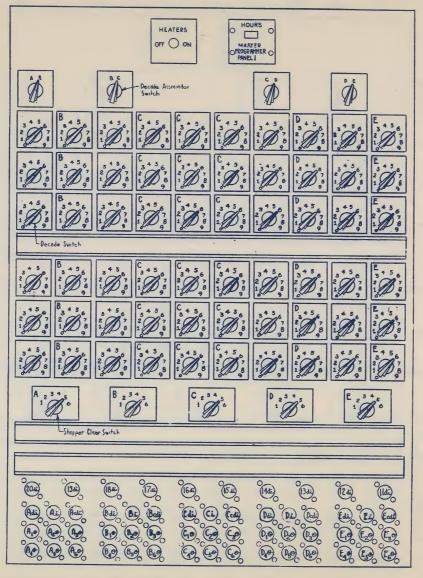

Stepper terminals

Decade terminals Dd120,....Ddi1

A1,....,Ki
Ano,....,Ko:
Stepper program pulse input terminale
Ad1....,Kdi
Stepper direct input Stepper clear direct input terminals

Decade direct input terminals

General Explanation of Steppers and Decades

- A stepper is a six stage ring counter. It has the following associated with it;
 - 1) Stepper program pulse input terminal
 - 2) Six stapper program pulse output terminals, one associated with each stage of the stepper.
 - 3) A group of decades (of from 0 to 5, depending upon the stepper and the settings of the decade associator switches. The n (m20,...,5) decades of each group are inter-connected by a direct carry-over circuit (there is no delayed carry-over circuit) enabling them to count (not accumulate) 10 n = 1 pulses.
 - Stopper clear switch
 - Stepper direct input terminal
 - Stepper clear direct input terminal
 - 7) Each decade has a direct input terminal

The operation of a stepper and its associated equipment is as follows:

At the end of the initial clear each stepper is left on the 1st stage and each decade

Suppose a program pulse is received on a stepper program pulse input terminal. One Suppose a program pursue is leave to a program pulse is emitted from the program pulse output terminal cor-responding to the stage the stepper is on at the time it is emitted and a program pulse is sent to the units dec

Whenever a group of decades counts to the number set on those decade switches corresponding to the position of the stepper, one addition time later these decedes are cleared to zero and the stepper is either stepped to the next position, or (if it is on the position set on its stepper clear ewitch) cleared to the first position. Though the decedes will count either program pulses or digit pulses, any pulse which might cause this clearing and stepping action must be a program pulse.

The decades count both the pulses supplied to the associated stepper's program pulse input terminal (with a one addition time delay) and those supplied to the decade direct input terminals. No set-up is permissible which might lead to pulses being supplied to a decade from both sources simultaneously, or from a decade direct input terminal and a carryover from a previous decade simulteneously.

An example flustrating a common application of a stepper in programming will show how items 1 through 4 operate together. Consider stepper D, and suppose that decades 12 and 13 are associated with it and that its stepper cleer switch is set to 4. Then four two-digits numbers (n1 nk) may be set up on the decade switches, each number associated with the corresponding stage (1....4) of the stepper and hence with the corresponding program pulse output terminale (D₁₀,..., M₂₀). Menewer a program pulse size received on D₁ a pulse is emitted from one of the output terminale (one addition time lator). The first n₁ pulses received on D₁ are emitted from D₂₀,..., the last n₁ pulses received on D₁ are emitted from D₂₀,..., the last n₁ pulses received on D₁ are emitted from D₂₀, and the stepper and its associated from D₂₀, and the stepper and description from D₂₀, and description from D₂₀, and description from D₂₀, and description fr ciated decades ere then left in their original state, ready to repeat the process. The time schedule of these operations is as follows:

Program Pulse	Cperation
0	Input program pulse (to Di)
1	Output program pulse emitted (from D10,D40)
	Decede stepped to next stage
2	In case the decades register the number set up on
	the decade switches, all decedes (associated with
	stapper D) are classed to zero and the stapper (I
	is stepped to the next stage or (if it is on the
	position II) it is alonged to the first stage

To disassociate a decade from its stepper pull out gate tube 63 in the stepper plug-in unit. See block diagram PX-6-304.

Terminels Ai, Bi.......Ki Stepper program pulse input terminals Stepper program pulse output terminals associated with Stage 1 Stage 2.....


Stege 6 One addition time after a program pulse is supplied to an input terminal (such as Di)

a program pulse is enitted from the output terminal corresponding to the steep the stepper is on at the time it is emitted (thus if the stepper is to position 4, when the pulse is emitted it comes from Doj, and a unt is added to the contents of the escalated decades.

Stepper clear direct input terminals.

A pulse supplied to this terminal will clear the stepper to the first position. If a clearing pulse and a stepping pulse errive at the same time, the stepper will be cleared, not

MOOR			ELECTRICAL OF PENNSYLE						
MASTER	PROGR	PAMMER	FRONT PANEL	NO.1					
MATERIAL			FINISH	SCALE					
Drawn by: JEDELSACK DEC.1944		ed by:	Approved by:	PX-8-301					

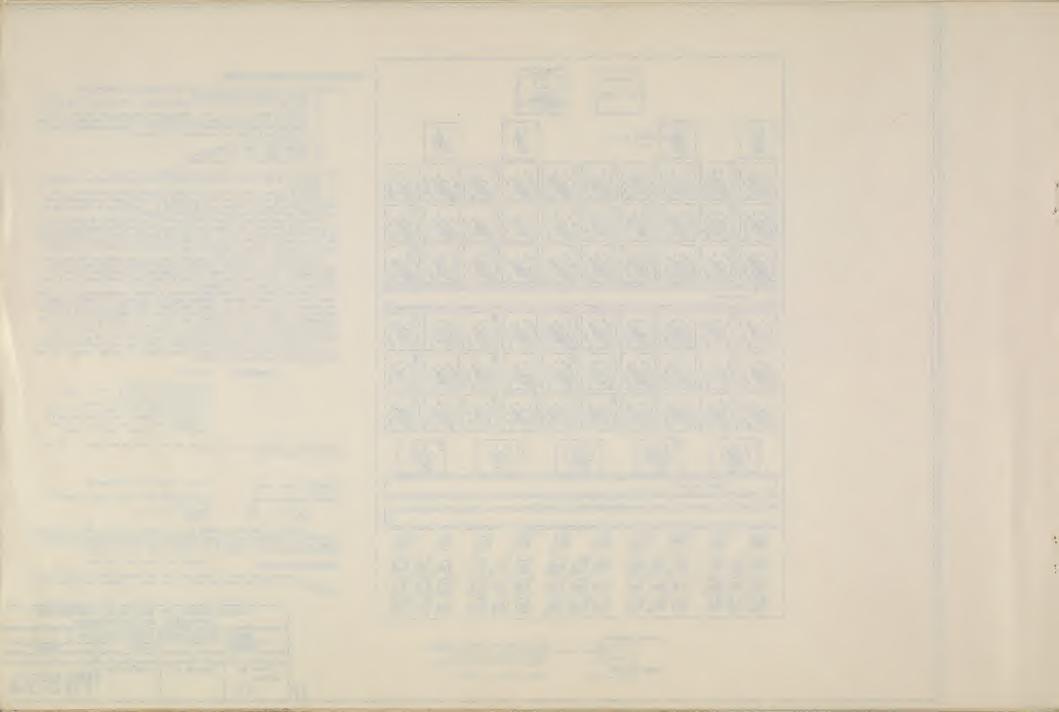

Switches Decade 2 HOURS HEATERS OFF ON OPROGRAMMER O TERMINALS 1di, 2di,, 20di - Decade direct input terminals apsociated respectively with decades 1, 2,...., 20. (counted from right to left)

Pulses supplied to these terminals will be counted by the decades. These pulses may be either program or digit pulses, though any pulse which steps the decades to the number set up on the decades switches corresponding to position of the stepper must be a program pulses, and any pulse which cames a carry-over must be a program pulses. Ro program pulses should be supplied to the decade direct input of the units decade of a temper one eddition time following the reception of a program pulse on the program pulse input terminal of that stopper considering the reception of a program pulse on the program pulse input terminal of the direct input terminals of decades other than the units decade only at times when there

are no carry-over pulses from previous decades of the set.

To disassociate a decade from its atempar pull out gate tube 63 in the stepper plug-in unit - See Block Diagrem PX-K-304.

Decade Associator Cwitches
Decades provided with those switches may be connected to the decades associated with either of two
steppors. Thus if the J-K switch is set to K, decade 2 is connected in series with decade 1, while if it
is set to J decade 2 to made the units decade associated with stapper J, and decade 3 (formerly the units decade associated with that stepper) becomes the tens decade of that stepper, i.e., is put in series with decade 2.

Decade switches associated with the 1st stages of the steppers.

Decade switches associated with the 2nd steges of the steppers.

Decade switches associated with the 3rd stages of the steppers.

. Decade switches associated with the 4th stages of the steppers.

- Decade switches associated with the 5th stages of the steppers.

Decade switches associated with the 6th stages of the steppers.

Stepper clear switch

This switch determines the number of steges of the stepper and associated decade switches which are used. After the stepper gets to the stage set on its clear switch and counts to the number set on the corresponding decade switches it clears to its first position instead of stepping to the next position.

Terminals Adi.....Kdi - Stepper direct input terminals.


Fulses supplied to one of these terminals will be counted by the stepper. These pulses may be either program pulses or digit pulses. If digit pulses are used the stenner cleer switch must be set to 6.


The stepper will count modulo c, where c is the setting of the stepper clear switch.

A program pulse is emitted from one of the stepper program pulse output terminals one addition time after a program pulse is received on the stepper program pulse inout terminal. This pulse is emitted from the terminal corresponding to the state of the stepper at the time it is emitted. The stepper may be stepped or cleared at the same time without effecting that pulse.

No pulse should be supplied to this terminal at the same time as a stepping action is caused by the

	MOOR			ELECTRIC OF PENN		ENGINEERING IANIA				
	MASTE	R PROG	RAMME	R FRONT	PAN	EL NO. 2				
	MATERIAL			FINISH	SCALE					
1	Drawn by: J.EDELSACK DEC. 1944	Chatso (1 U)	od oy:	Approved	by:+	PX-8-302				

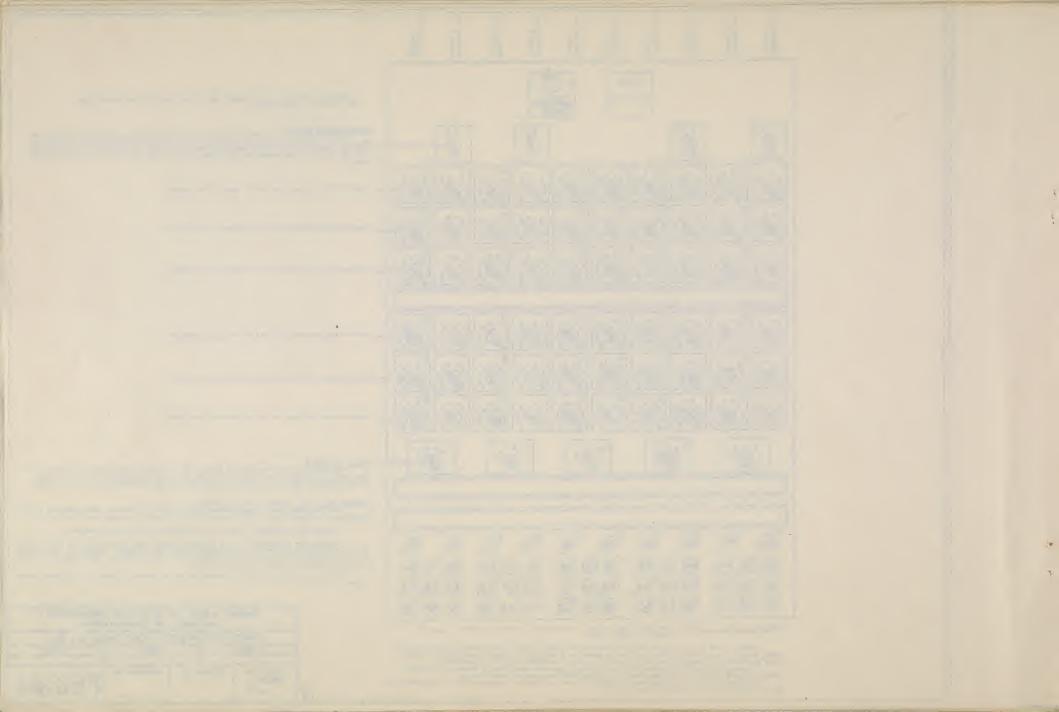

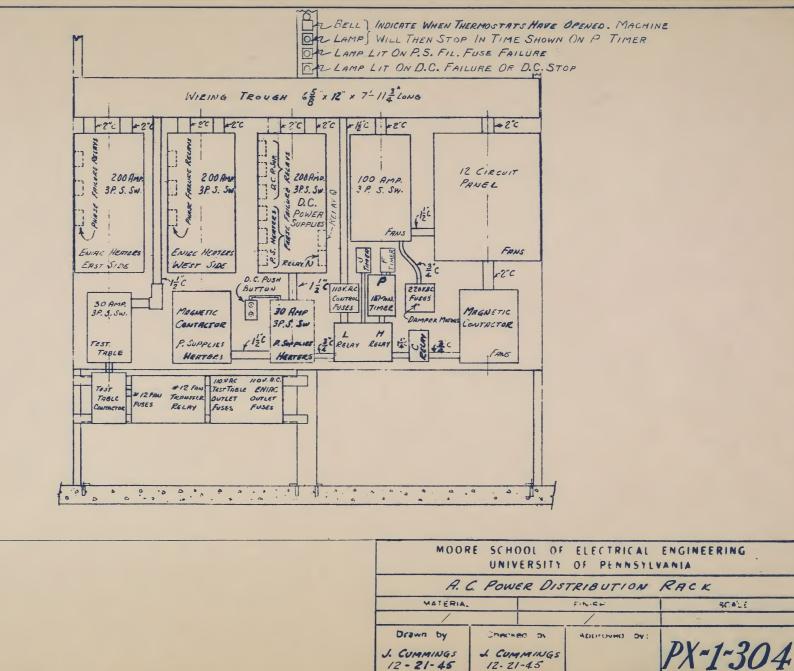

REVISIONS

F.F. F. TIMERS REVI R. RELAYS, INDICATE

ANYES & BELL ALDER

